

Creating a Prototype Traction Motor Inverter

AMF-ACC-T1655

Neil Krohn | Distinguished Member Technical Staff E/V Systems

SEPT. 2015



External Use

Freescale, the Freescale logo, AllWin, C-S, CodeTEST, CodeWarrior, ColdFire, ColdFire+, C-Ware, the Energy Efficient Solutions logo, Kinetic, MagniV, motorGT, PEG, PowerQUICC, Prosecc Expert, QorIQ, QorIQ Qonvergence, Qorivos, Ready Plus, SafeAssure, the SafeAssure logo, StarCore, Synchrify, Vortiga, Vybrid and Xilinx are trademarks of Freescale Semiconductor, Inc., Reg. U.S. Pat. & Tm. Off. AirMat, BeeKit, BeeStack, CoreNet, Flexis, LayerStack, MXC, Platform in a Package, QUICC Engine, SMARTMO25, Tower, TurboLink and UMEMS are trademarks of Freescale Semiconductor, Inc. All other product or service names are the property of their respective owners. © 2015 Freescale Semiconductor, Inc.



Agenda

- EV/HEV History at Motorola / Freescale
- Automotive High Power IGBT Product Overview
- Introduction to Induction Motors
- Description of Freescale's Automotive EV/HEV Inverter
- Inverter Testing using Basic V/F Motor Control
- V/F Freq. & Voltage Waveform Generation
- Dead Time Generation Discussion
- Advanced IGBT GDIC Description
- Gate Drive Board and Schematic Overview
- IGBT Switching Characteristics and Challenges
- Advanced Gate Drive IC Concepts



Many Years of EV Experience Since Early 1990's

- Dodge Dakota
- GVW 6020 lbs
- 324V Battery Pack
- 24 -12V Gel-Cells
- 1 -12V Aux Battery
- 50HP Continuous
- 140HP Peak
- 24 -12V Gel-Cell
- 1750 lb Battery Pack
- Motorola Designed 300A 400V Inverter
- On-board Opportunity Charger



DRIVING AUTOMOTIVE ELECTRONICS

DRIVING AUTOMOTIVE ELECTRONICS



1994 Ford Custom 400A 600V IPM Half Bridge

78 002 443110 98-01-00
CAP DESIGN: EV Howell

3-15-94

And, we would like to
a connector like the one shown
below for the control leads.

It would be part of the cap and would protect the
control leads much more than what Mitsubishi currently
does. Please give me inputs on dimensions x, y, & z below.
Thickness t will be
about .060".

Upon receipt of
your feedback,
I will design
this connector
into the cap.

Cost Budget:
New Design


Question
* Connect
handling for
Vcc & GND? 2 pins or 1?

* Key mechanism to
avoid putting it in wrong?
* Snap fit mechanism?
Control
lead connector

* "Auto Modular Connector" is used now.
002 807 430312 2 / 2
3-15-94 1:08PM

M. P. ...
TAS INDS

Déjà Vu

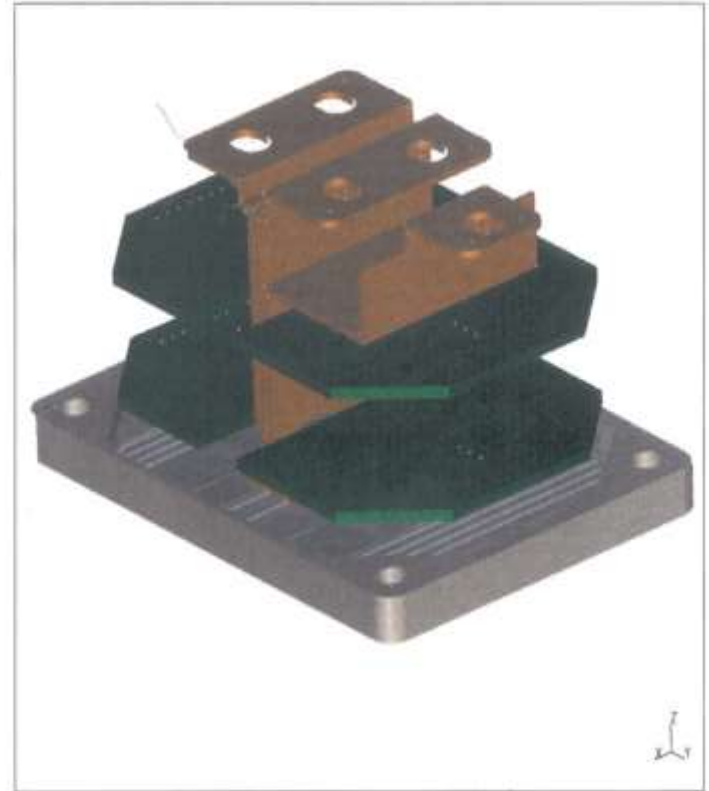

Now Back to The Future



Freescale Uniquely Positioned To Address HEV/EV

Start Stop

- Drivers
- Re-Gen Braking
- Power Devices



LV Battery Monitoring

- MCU
- Voltage Monitoring
- Packaging




HV Battery Management

- MCU
- Charge Monitoring
- Charge Balancing
- Communications
- Isolation

Inverter

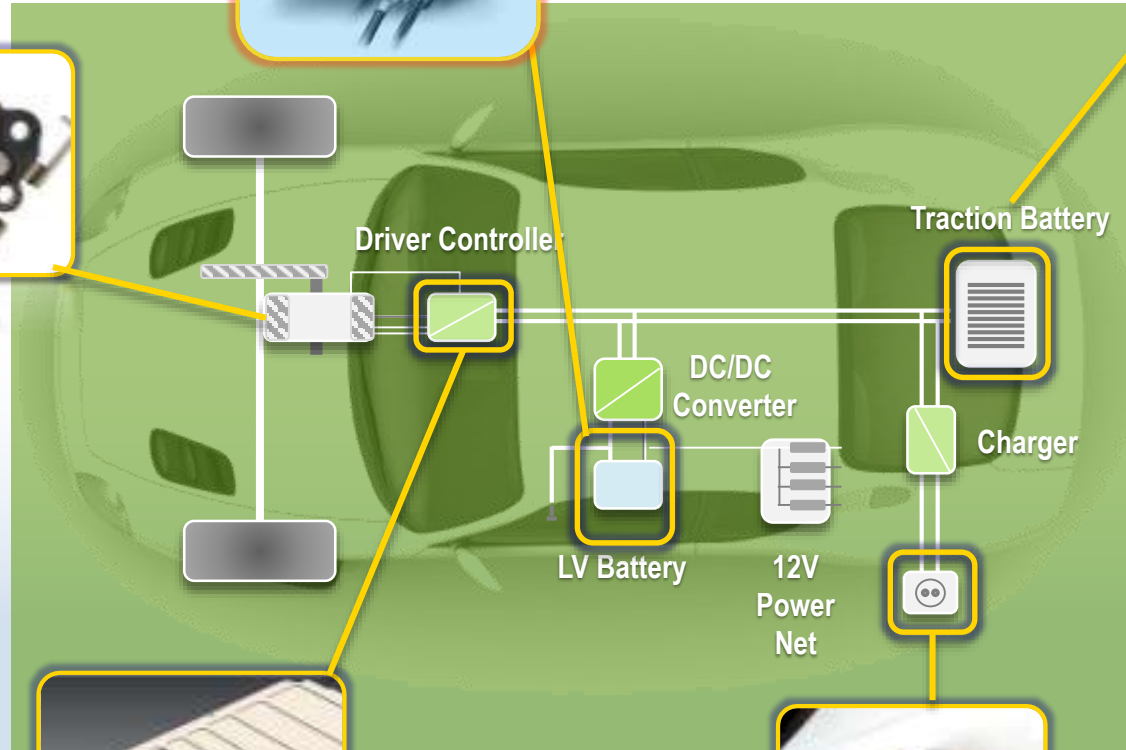- Control & Safing MCU
- Isolation
- Drivers
- Power Devices
- FOC Software
- Modeling and Simulation Tools



Charge Point


- MCU
- Communications



High Voltage Motor Dynamometer LAB in Phoenix

EV team in Phoenix with the necessary skills to do:

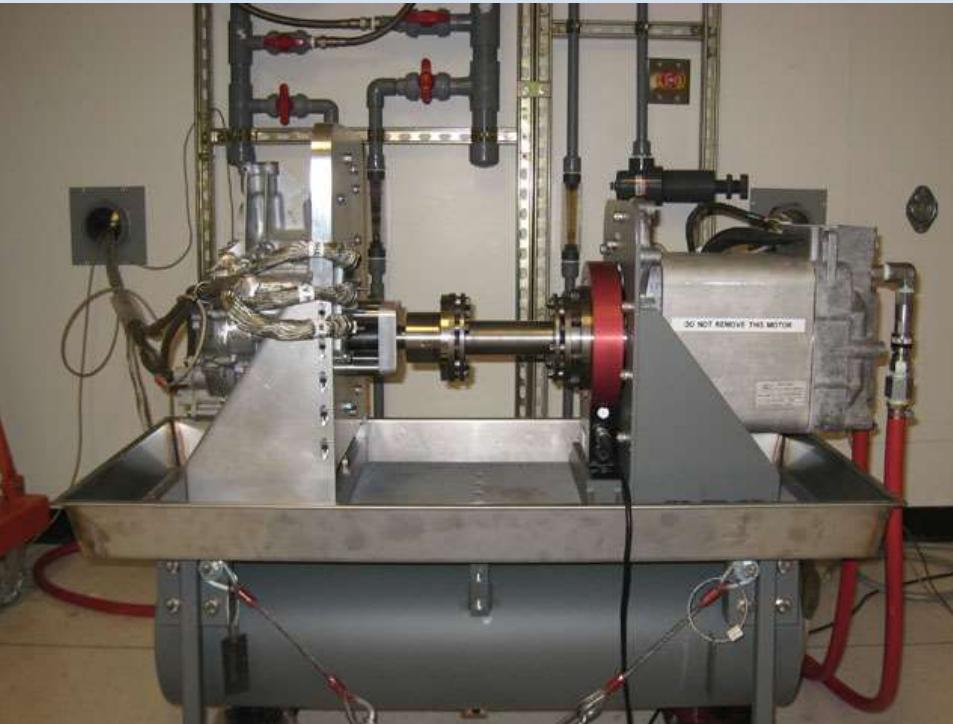- Competitive analysis / existing product evaluation
- Validating new ideas / inventions IP & patents
- Define new potential products. Provide requirements / prototypes
- Help with evaluation of potential partners / acquisitions
- Integrate products / leverage ideas from across the Corporation
- Provide an environment for rapid prototyping
- Testing / making business case on new concepts



Continuing To Build On Our Real World Experience

Freescle Designed

- Controller Board
- Gate Driver Board
- Common Mode Filter Board
- Motor Control Software
- Enclosure



65kW Prototype Inverter Developed for an Auto OEM

Partnering Provides FSL Quick Market Access

What We Were Seeking:

- Access to auto qualified IGBT, Diode components, modules
- Influence over IGBT, module roadmap
- Ability to get to market quickly
- Profitable cooperation model
- Security of supply

Potential Partners

Semikron

Packaging
Modules



Danfoss

Packaging
Modules
Cooling




MaxQ

Cold plates



Fuji Automotive IGBTs

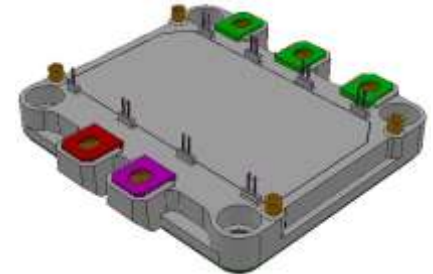650V / 400A Half H Bridge
High speed switching
Low inductance module structure



Freescale Semiconductor and Fuji Electric partner to increase efficiency of hybrid electric vehicle

Freescale enhances its powertrain portfolio with Fuji Electric IGBT technology to help improve automotive industry's 'miles per watt'

AUSTIN, Texas –April 11, 2011 – Freescale Semiconductor has entered into a strategic alliance with Fuji Electric Co., Ltd. to collaborate on insulated-gate bipolar transistor (IGBT) technology and products for hybrid electric and electric vehicles (HEV and EV). Working with Fuji Electric, Freescale will add high-power IGBT products to its existing portfolio of solutions for electronic powertrain applications, market those products to its automotive customers and define and produce new products based on customer input.

IGBTs are currently the largest segment of the market for EV power systems. With the addition of IGBTs to its portfolio, Freescale will offer all of the major electronic components of EV systems, including microcontrollers, analog gate drivers, battery monitoring ICs, power IGBTs and modeling / simulation tools, and software components / tools for motor control development.

The IGBT is a high-voltage, high-current switch connected directly to the traction motor in a hybrid electric or electric vehicle. It takes direct current energy from the car's battery and, through the inverter, converts the alternating current control signals into the high-current, high-voltage energy needed to commute or turn the motor. The IGBT is an ideal motor inverter switch for 35 KW to 85 KW EV motors due to its high efficiency and fast switching. The more efficient the IGBT, the less power is lost to wasted heat, resulting in better mileage or "miles per watt" (MPW) of energy.

"Freescale chose Fuji Electric's IGBT technology based on its high-performance characteristics and capability," said Tom Deitrich, senior vice president and general manager of Freescale's RF, Analog and Sensor Group. "Coupled with Freescale's automotive portfolio and pedigree, this alliance accelerates our ability to provide automotive customers with higher-efficiency inverter solutions."

"We are pleased to work with Freescale on IGBT technology and draw on their automotive capability. This alliance will enable our IGBT technology to contribute to the increased efficiency of electric vehicles," said Kuniaki Yanagisawa, executive officer and general manager of Fuji Electric's Electronic Devices Business Headquarters.

Freescale is a leader in the automotive semiconductor industry with a successful legacy in powertrain electronics. With its microcontrollers designed into many EV systems today, Freescale is well-positioned to supply customers with IGBTs and other devices that will be critical to the advancement of the electric vehicle.

About Fuji Electric

Fuji Electric is a leading company providing solutions for Energy and the Environment with its wide variety of products. Power semiconductors, one of its competitive product categories, are essential in the reduction of energy consumption in electric vehicles, industrial machines and home electronic appliances. Further information is available at Fuji Electric Group web site: <http://www.fujielectric.com>

About Freescale Semiconductor

Freescale Semiconductor is a global leader in the design and manufacture of embedded semiconductors for the automotive, consumer, industrial and networking markets. The privately held company is based in Austin, Texas, and has design, research and development, manufacturing and sales operations around the world. www.freescale.com.



Hybrid Vehicles installed Fuji's IGBT products

Our IGBTs are adopted for many type of vehicles

- Fuji IGBTs are used in **half of the Japanese EV/HEV market** except Prius, and a **quarter of whole Japanese EV/HEV market including Prius**

1995

Today



Lexus
GS450h



Lexus
LS600h
(2007)



Lexus
RX450
(2009)



Hino
Dutro



Toyota
Crown



Lexus
HS250h,
SAI



Nissan
Altima



Toyota
Camry



Toyota
Estima



2 in1 Intelligent Power Module



Production
Buck boost converter

Company T : HEV

SOP from 2005



14 in1 Intelligent Power Module



Production
2 Inverters
with buck boost
converter



Company H : HEV/PHEV



Power chip for double side cooling system


Production
Power chip by Fuji

Company D⇒T : HEV

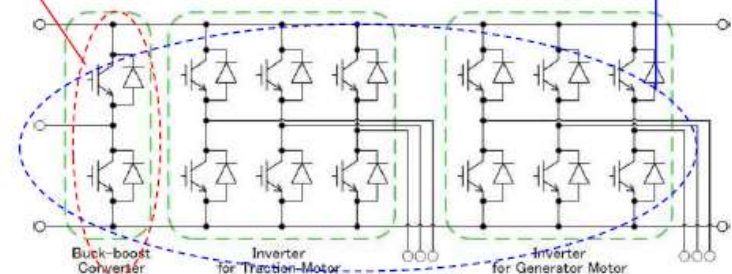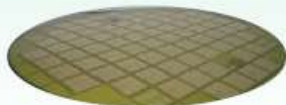


Standard Product Roadmap

Samples Now

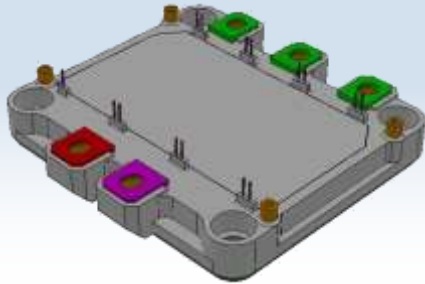


Voltage: 650V
Current: 400A

Samples Now

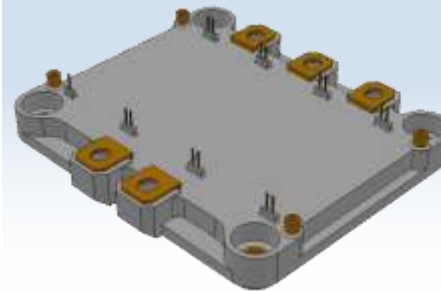

Voltage: 650V
Current: 600A

Samples Now

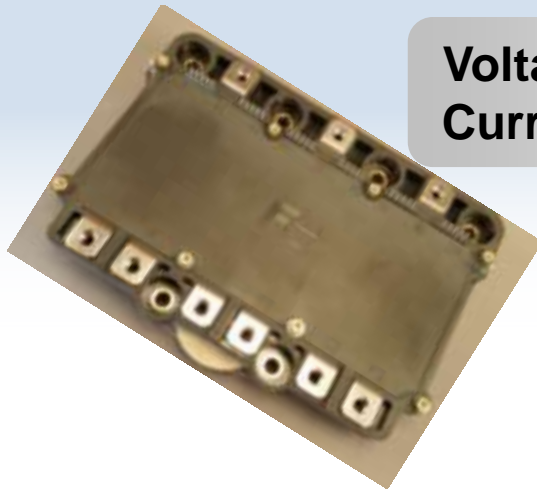

Voltage: 750V
Current: 800A


Production: 500K / Yr @ 0.0 PPM



Voltage: 1200V
Current: 600A

Fuji IGBTs Auto Applications

Boost Converter IPM (DC-DC Converter)

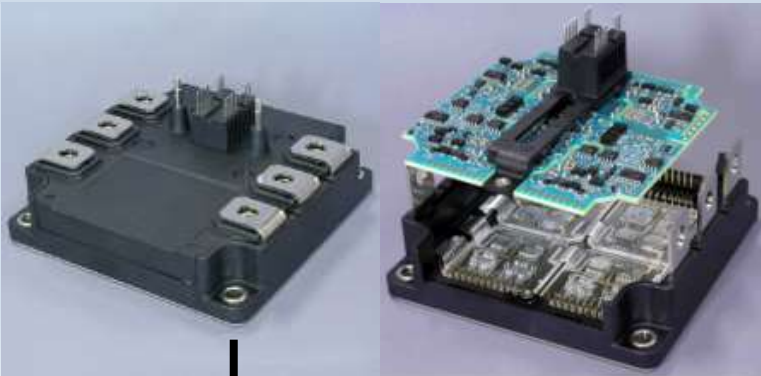


1200V/ 600A 2in1

Integrated IGBT Module

Since 2005

Volume
500K /
Yr @ 0.0
PPM

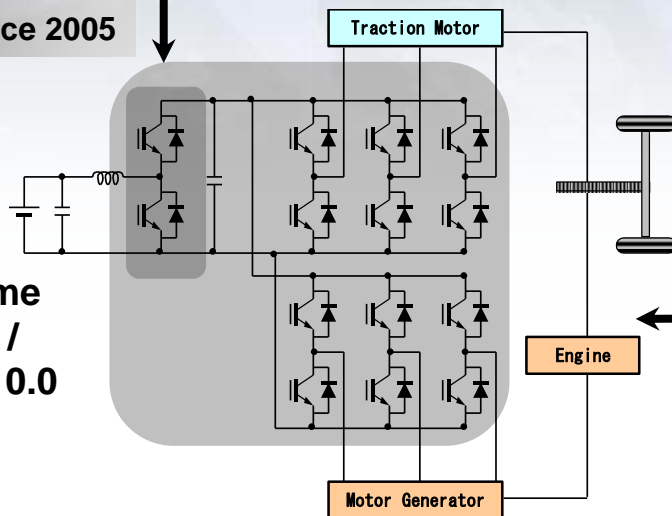

IGBT Wafer




Power chip
by Fuji

Module

1200V/ 400A 1in1


Since 2007

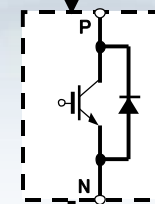

PCU



Ford Hybrid Electric Powertrain

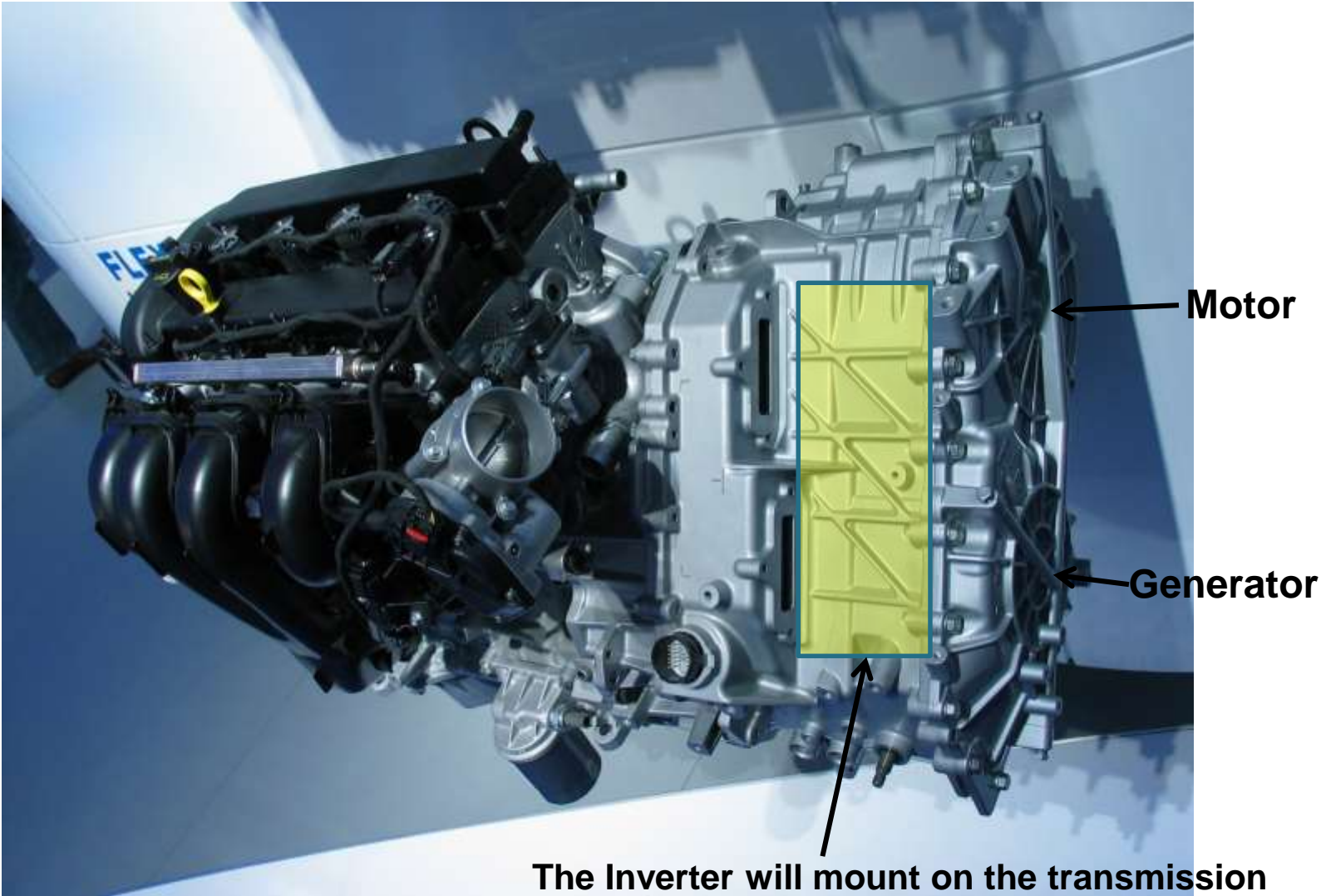


The Induction Motor and V/F Control




Induction Machines

Invented over a century ago independently by Nikola Tesla & Galileo Ferraris

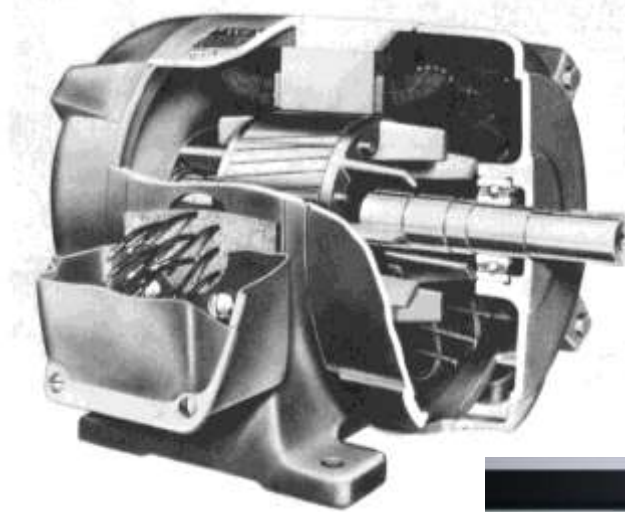- Stator same as BLDC
- Difference in rotor construction
- If properly controlled provides constant torque
- Low torque ripple
- No permanent magnets
- Think of it as a rotating transformer.
- Stator is the primary
- Rotor is the secondary
- Rotor current is “induced” from stator current



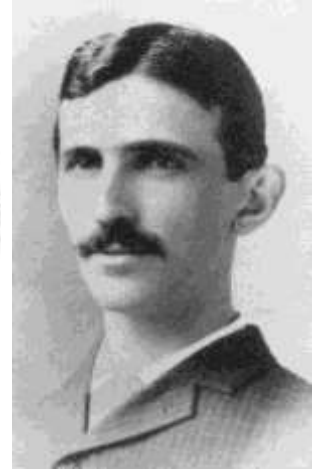Galileo Ferraris
GALILEO FERRARIS
NATO A CANTÙ (VARESE) IL 25 OTTOBRE 1857
MORTO A TRIESTE IL 7 OTTOBRE 1927.
Da una fotografia di Ettore di Giorgi.




Model of Tesla's 1st Induction Motor Demonstrated 1885



AC Induction Motor Slip


- Basic Principle:
 - The **stator** is a classic three-phase stator with the winding displaced by 120°
 - The **rotor** is a squirrel cage rotor in which bars are shorted together at both ends of the rotor by cast aluminum end rings
 - The rotor currents are **induced** by stator magnetic field.
- The **motor torque** is generated by an interaction between the stator magnetic field and induced rotor magnetic field

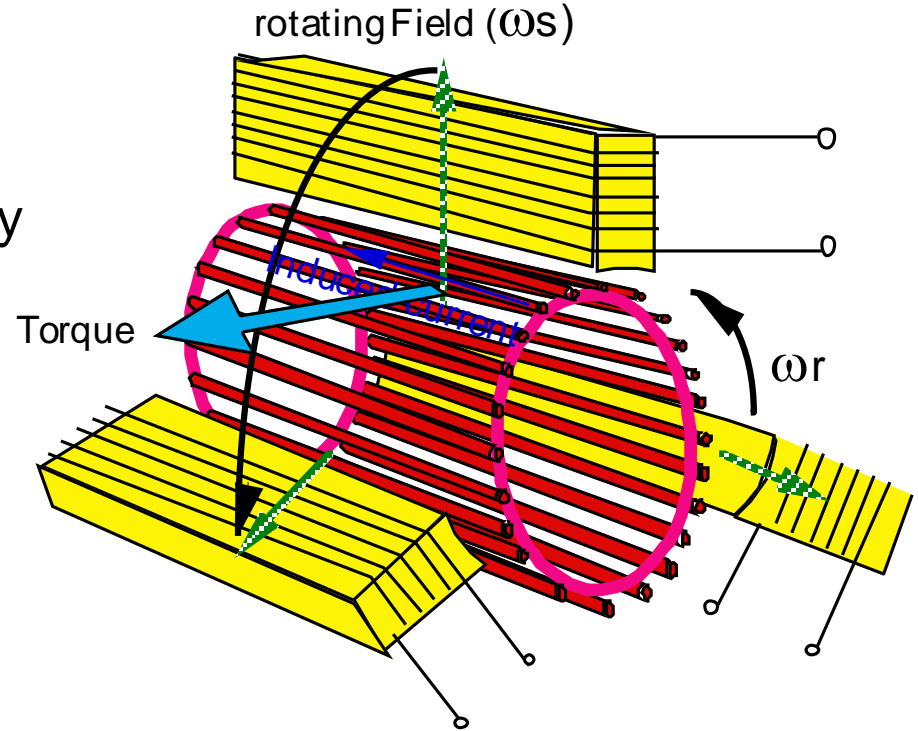

NO BRUSHES, NO PERMANENT MAGNETS

AC Induction Motor

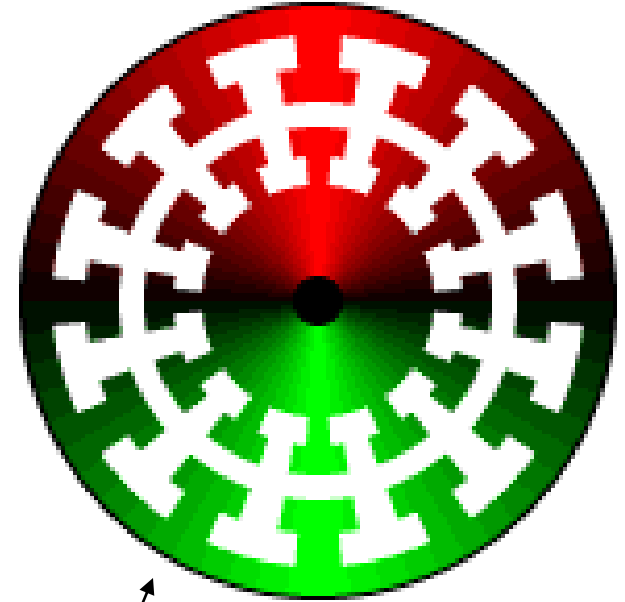- The **STATOR windings** are distributed around the stator to produce a roughly **sinusoidal distribution**.
- When three phase ac voltages are applied to the stator windings, a rotating magnetic field is produced.
- The **ROTOR** also consists of windings or, more often, a **copper squirrel cage**.
- An electric current is **induced** in the rotor bars which also produce a magnetic field.



Notice the rotor slip!


The **Rotor** does not quite keep up with the **Rotating Magnetic Field** of the stator.

4 Quadrant Operation

Generating / Braking

If the rotating magnetic field is slower than the rotor speed & in the same direction, your generating & braking

Stator
Rotor

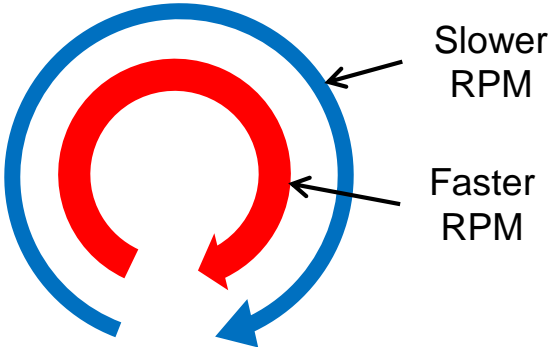


Driving


If the rotating magnetic field is faster than the armature speed & in the same direction, your driving




Driving

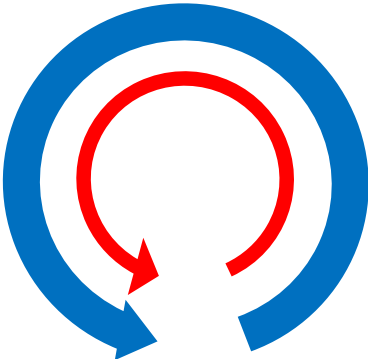

Generating / Braking

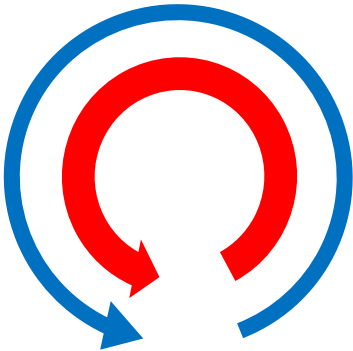

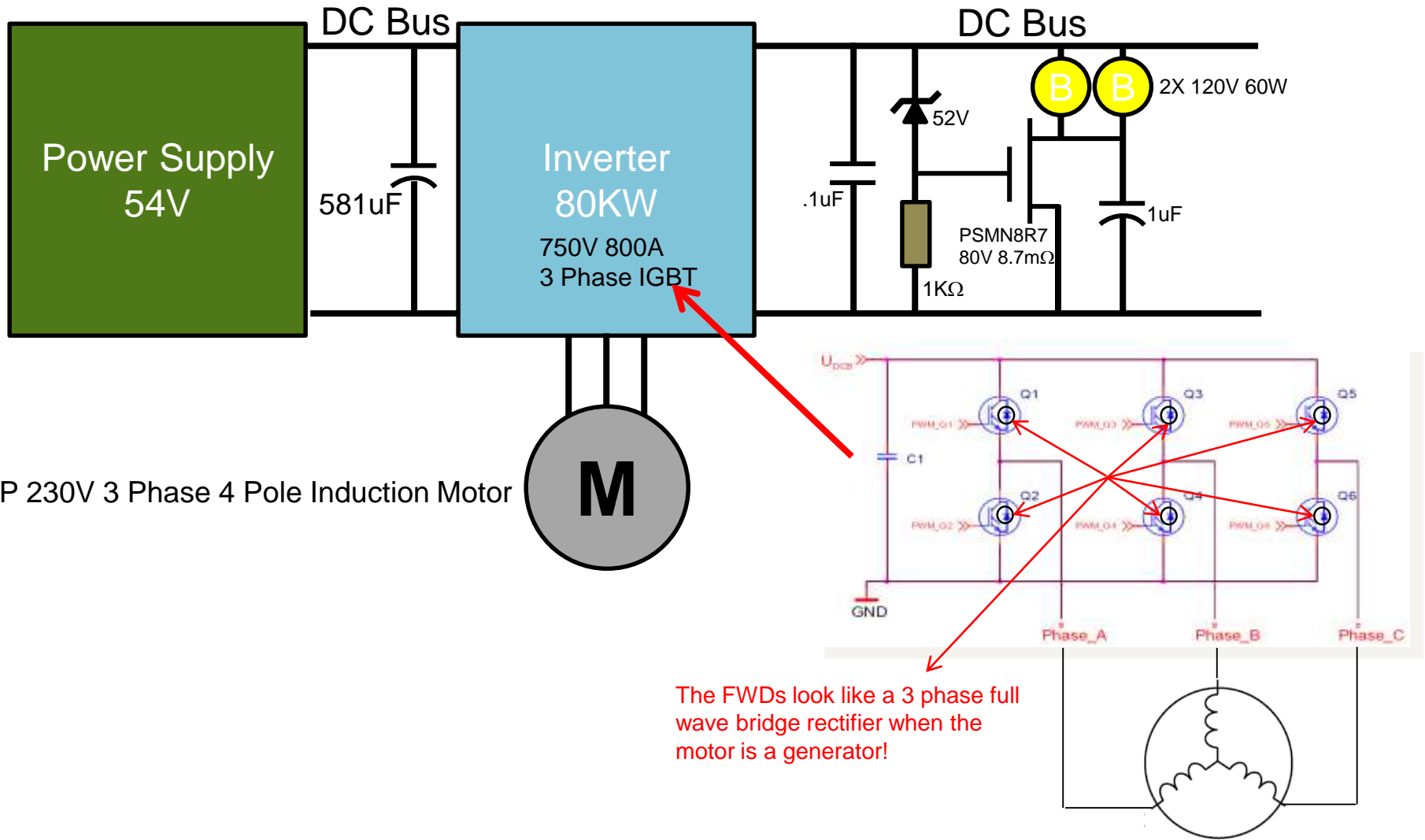Regeneration and Braking on the Test Inverter



1HP 230V 3 Phase 4 Pole Induction Motor

The FWDs look like a 3 phase full wave bridge rectifier when the motor is a generator!

RPM and Slip Equations

$$n_s = \frac{120 \times f}{p}$$

n_s = synchronous RPM

f = freq in Hz

p = number of motor poles

$c = 120 = 2 \times 60 \rightarrow 2$ converts pole pairs to poles & 60 converts Hz to RPM

Ex. 1hp 3 phase 4 pole motor running at 60Hz $120 \times 60 / 4 = 1800$ RPM

- Slip is defined as the difference between the synchronous or stator (magnetic field) and the armature speed.
- Slip can be expressed as a percentage or RPM

$$s = \frac{n_s - n_r}{n_s}$$

s = slip


n_s = stator speed

n_r = rotor speed

Ex. @ 1725 RPM the above motor puts out full rated torque. That motor runs at 1800 RPM synchronously. $1800 - 1725 / 1800 = s = 4.1\%$ or $1800 - 1725 = 75$ RPM.



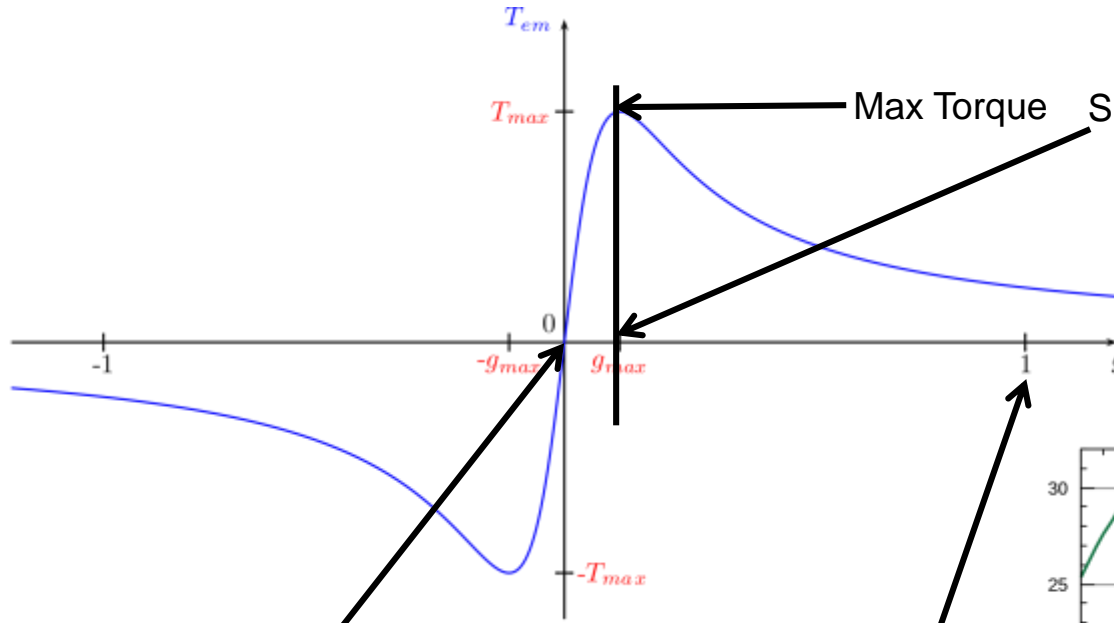Induction Motor Torque vs. Slip Relationship




Synchronous speed. Torque= 0 Slip = 0%


Armature is at 0 RPM slip = 100%

Slip can be stated as a % or RPM


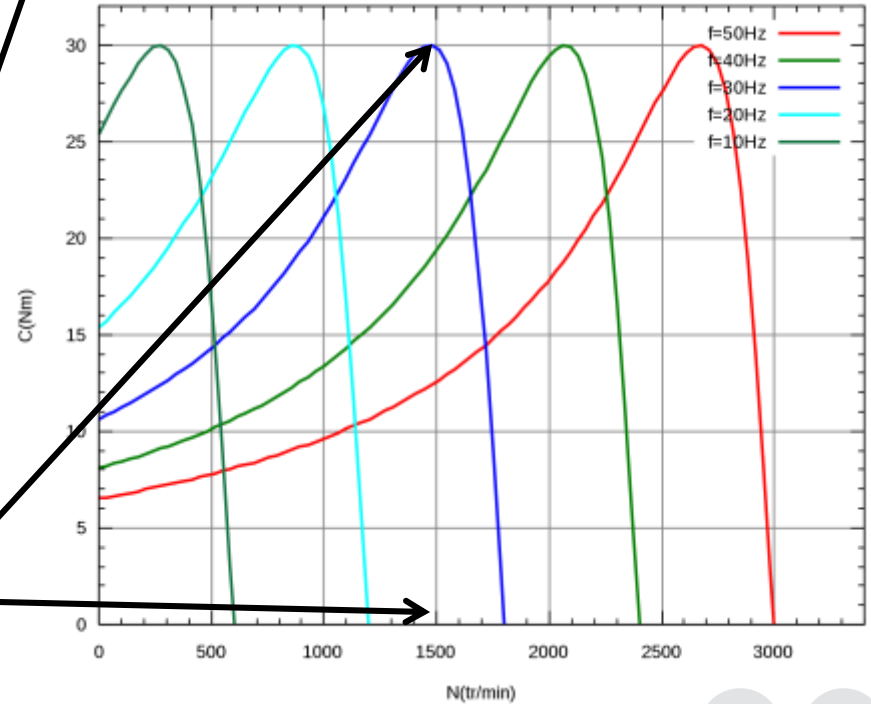
By changing Freq. & Voltage we can generate rated torque at any RPM




Sinusoidal PWM Generation – ACIM / PMSM

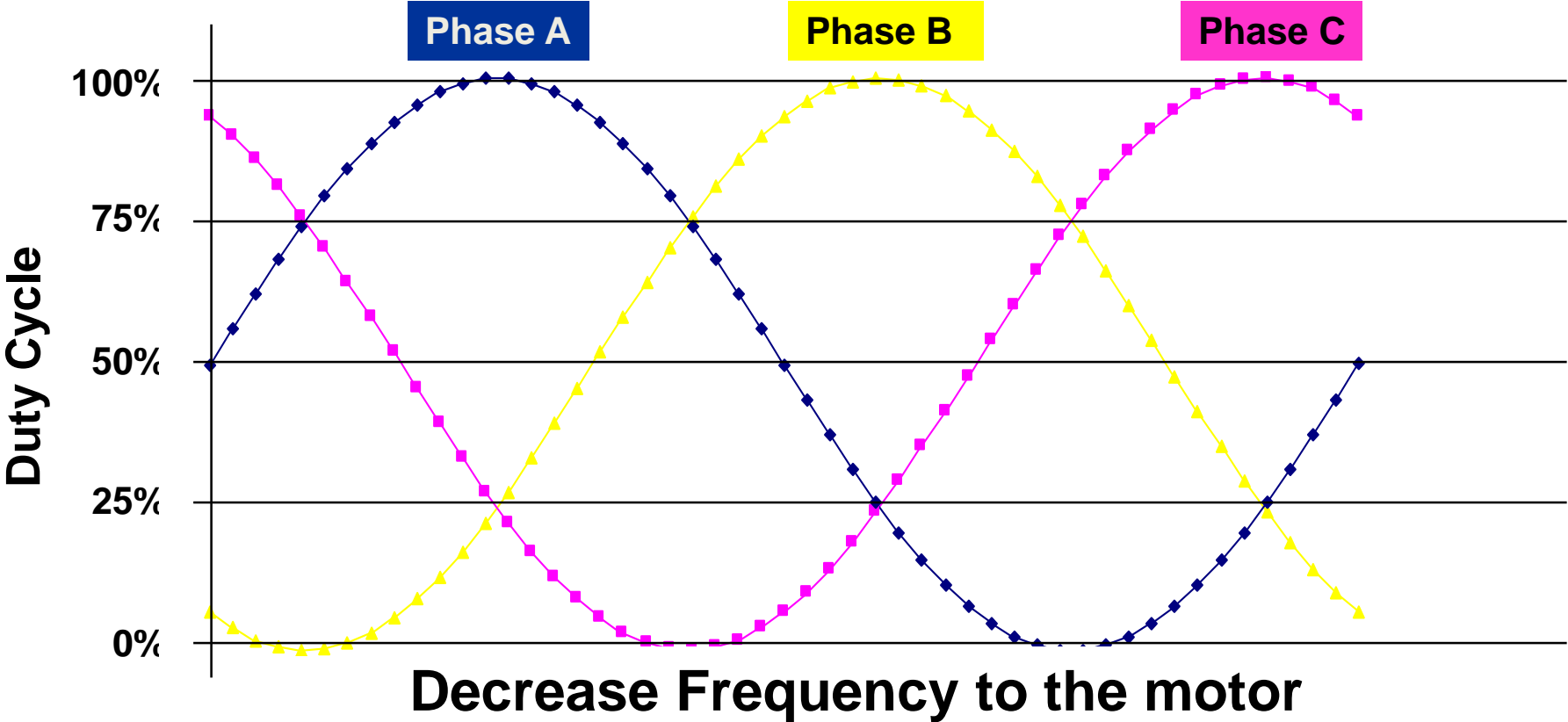



AC Sine wave from DC

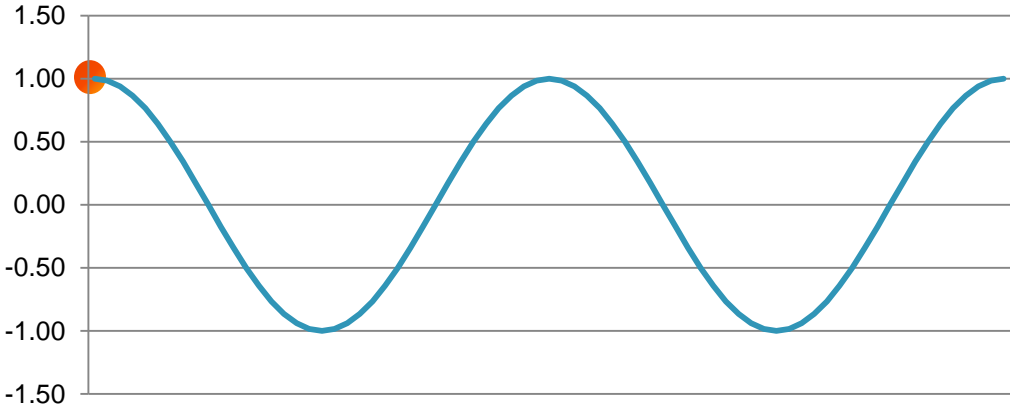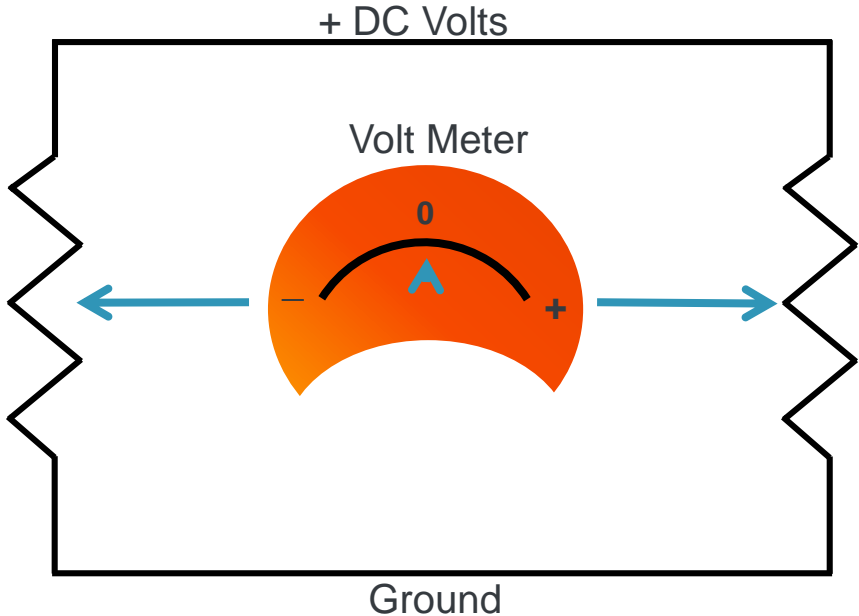

PWMing a Half H Bridge

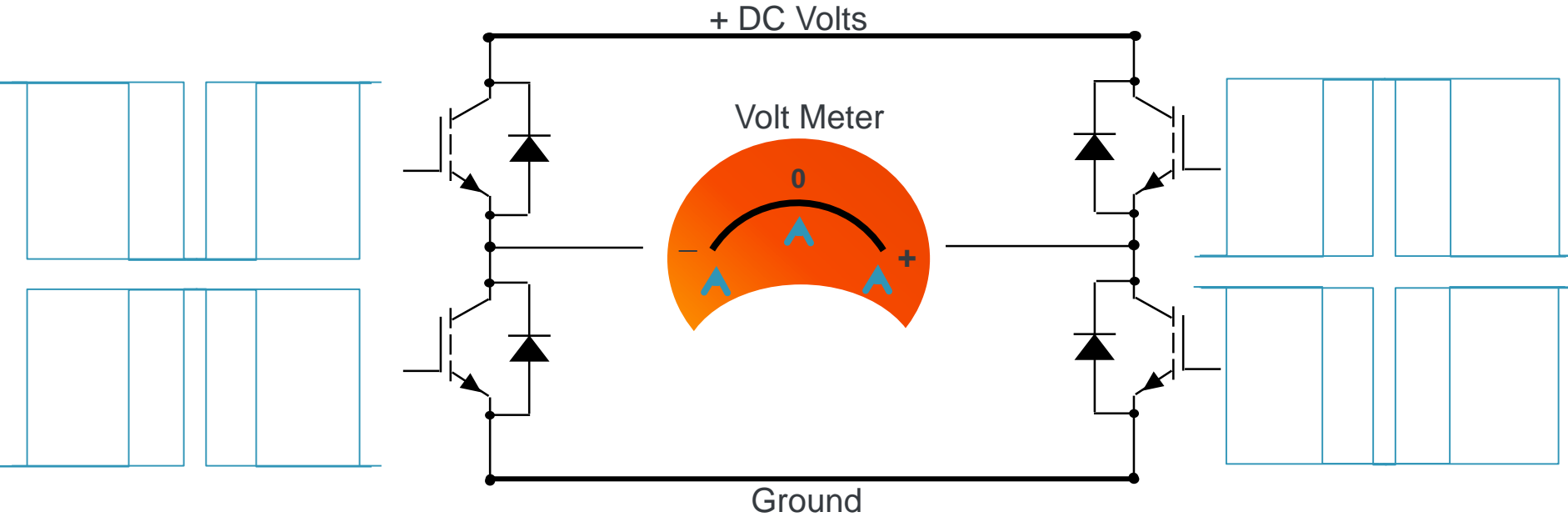



AC Sine wave from DC

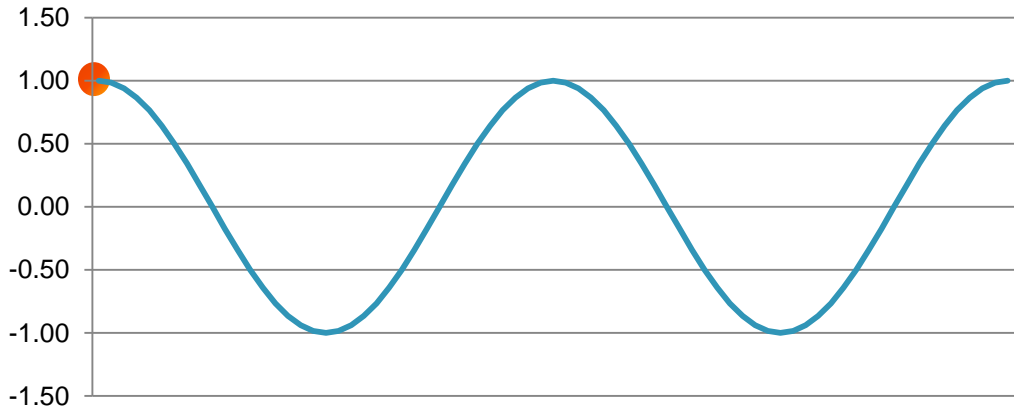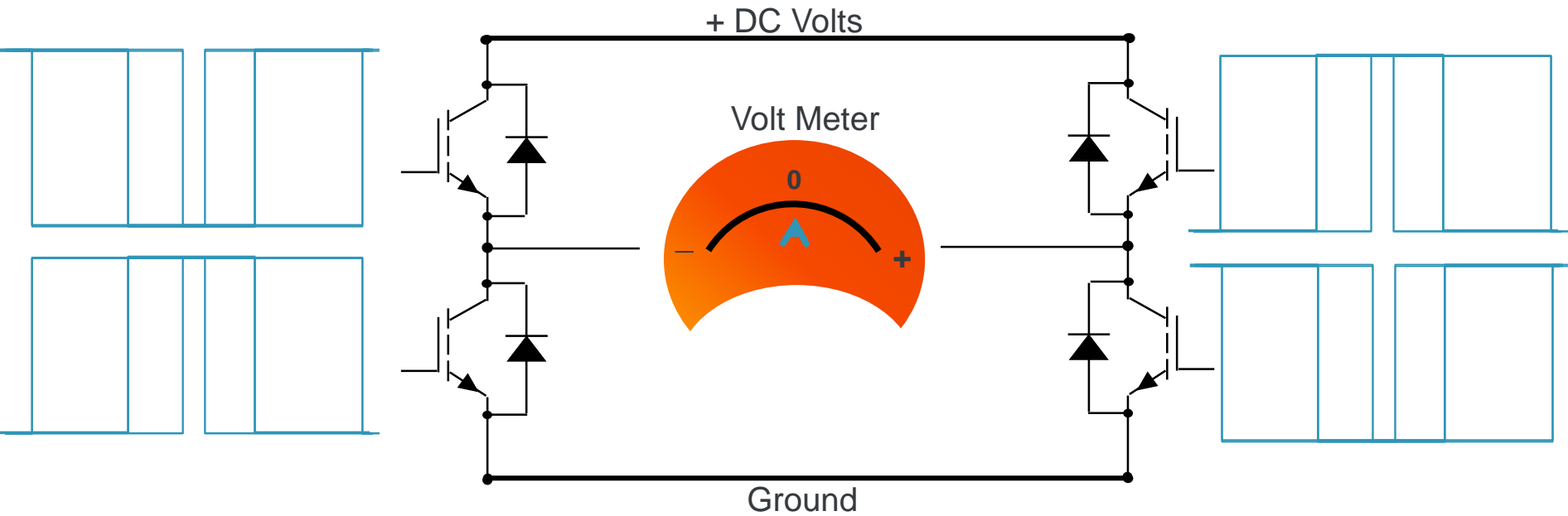

Simple Sine Wave Inverter


deg	rad	sin	scaled 255	hex	deg	rad	sin	scaled 255	hex
0	0.000	0.00	128	80	180	3.141	0.00	128	80
10	0.175	0.17	150	96	190	3.316	-0.17	106	69
20	0.349	0.34	172	AB	200	3.490	-0.34	84	54
30	0.524	0.50	192	BF	210	3.665	-0.50	64	40
40	0.698	0.64	210	D2	220	3.839	-0.64	46	2D
50	0.873	0.77	226	E2	230	4.014	-0.77	30	1E
60	1.047	0.87	239	EE	240	4.188	-0.87	17	11
70	1.222	0.94	248	F8	250	4.363	-0.94	8	7
80	1.396	0.98	254	FE	260	4.537	-0.98	2	1
90	1.571	1.00	256	FF	270	4.712	-1.00	0	0
100	1.745	0.98	254	FE	280	4.886	-0.98	2	1
110	1.920	0.94	248	F8	290	5.061	-0.94	8	7
120	2.094	0.87	239	EE	300	5.235	-0.87	17	11
130	2.269	0.77	226	E2	310	5.410	-0.77	30	1D
140	2.443	0.64	210	D2	320	5.584	-0.64	46	2D
150	2.618	0.50	192	C0	330	5.759	-0.50	64	3F
160	2.792	0.34	172	AB	340	5.933	-0.34	84	54
170	2.967	0.17	150	96	350	6.108	-0.17	106	69
180	3.141	0.00	128	80	360	6.282	0.00	128	7F
190	3.316	-0.17	106	69	10	0.175	0.17	150	96
200	3.490	-0.34	84	54	20	0.349	0.34	172	AB
210	3.665	-0.50	64	40	30	0.524	0.50	192	BF
220	3.839	-0.64	46	2D	40	0.698	0.64	210	D2
230	4.014	-0.77	30	1E	50	0.873	0.77	226	E2
240	4.188	-0.87	17	11	60	1.047	0.87	239	EE
250	4.363	-0.94	8	7	70	1.222	0.94	248	F8
260	4.537	-0.98	2	1	80	1.396	0.98	254	FE
270	4.712	-1.00	0	0	90	1.571	1.00	256	FF
280	4.886	-0.98	2	1	100	1.745	0.98	254	FE
290	5.061	-0.94	8	7	110	1.920	0.94	248	F8
300	5.235	-0.87	17	11	120	2.094	0.87	239	EE
310	5.410	-0.77	30	1D	130	2.269	0.77	226	E2
320	5.584	-0.64	46	2D	140	2.443	0.64	210	D2
330	5.759	-0.50	64	3F	150	2.618	0.50	192	C0
340	5.933	-0.34	84	54	160	2.792	0.34	172	AB
350	6.108	-0.17	106	69	170	2.967	0.17	150	96
360	6.282	0.00	128	7F	180	3.141	0.00	128	80

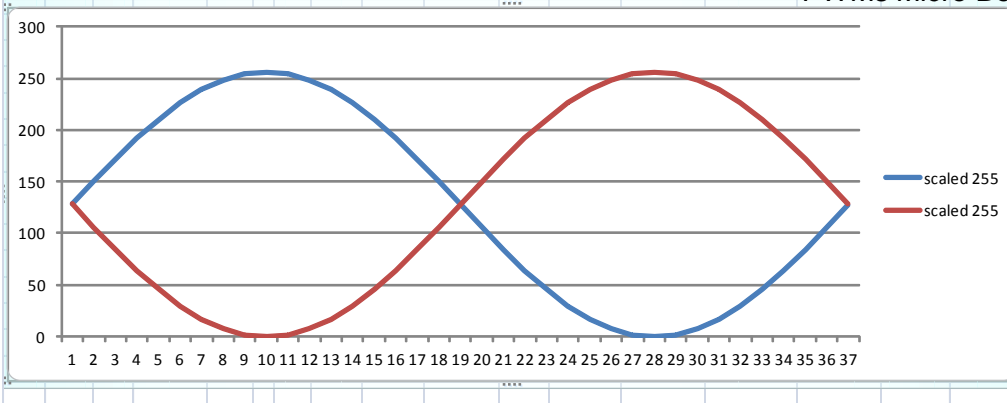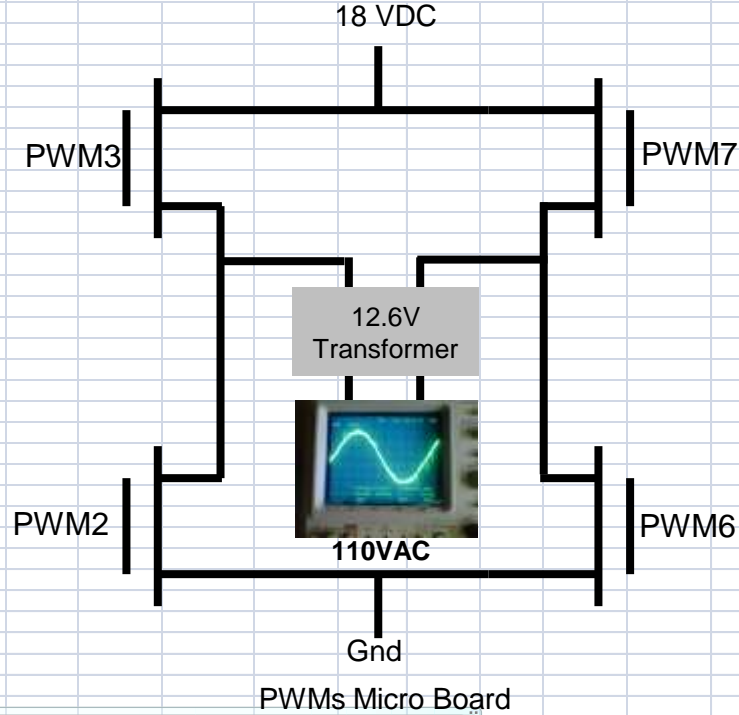This table generates sinwave PWMs used to produce an inverter sine wave on an H bridge
The lower PWM is inverted from the Upper PWM signal on the same 1/2 H



3 Phase Sine Wave Generation


deg	rad	sin	scaled 255	hex	deg	rad	sin	scaled 255	hex	deg	rad	sin	scaled 255	hex
360	6.282	0.00	128	7F	120	2.094	0.87	239	EE	240	4.188	-0.87	17	11
10	0.175	0.17	150	96	130	2.269	0.77	226	E2	250	4.363	-0.94	8	7
20	0.349	0.34	172	AB	140	2.443	0.64	210	D2	260	4.537	-0.98	2	1
30	0.524	0.50	192	BF	150	2.618	0.50	192	C0	270	4.712	-1.00	0	0
40	0.698	0.64	210	D2	160	2.792	0.34	172	AB	280	4.886	-0.98	2	1
50	0.873	0.77	226	E2	170	2.967	0.17	150	96	290	5.061	-0.94	8	7
60	1.047	0.87	239	EE	180	3.141	0.00	128	80	300	5.235	-0.87	17	11
70	1.222	0.94	248	F8	190	3.316	-0.17	106	69	310	5.410	-0.77	30	1D
80	1.396	0.98	254	FE	200	3.490	-0.34	84	54	320	5.584	-0.64	46	2D
90	1.571	1.00	256	FF	210	3.665	-0.50	64	40	330	5.759	-0.50	64	3F
100	1.745	0.98	254	FE	220	3.839	-0.64	46	2D	340	5.933	-0.34	84	54
110	1.920	0.94	248	F8	230	4.014	-0.77	30	1E	350	6.108	-0.17	106	69
120	2.094	0.87	239	EE	240	4.188	-0.87	17	11	360	6.282	0.00	128	7F
130	2.269	0.77	226	E2	250	4.363	-0.94	8	7	10	0.175	0.17	150	96
140	2.443	0.64	210	D2	260	4.537	-0.98	2	1	20	0.349	0.34	172	AB
150	2.618	0.50	192	C0	270	4.712	-1.00	0	0	30	0.524	0.50	192	BF
160	2.792	0.34	172	AB	280	4.886	-0.98	2	1	40	0.698	0.64	210	D2
170	2.967	0.17	150	96	290	5.061	-0.94	8	7	50	0.873	0.77	226	E2
180	3.141	0.00	128	80	300	5.235	-0.87	17	11	60	1.047	0.87	239	EE
190	3.316	-0.17	106	69	310	5.410	-0.77	30	1D	70	1.222	0.94	248	F8
200	3.490	-0.34	84	54	320	5.584	-0.64	46	2D	80	1.396	0.98	254	FE
210	3.665	-0.50	64	40	330	5.759	-0.50	64	3F	90	1.571	1.00	256	FF
220	3.839	-0.64	46	2D	340	5.933	-0.34	84	54	100	1.745	0.98	254	FE
230	4.014	-0.77	30	1E	350	6.108	-0.17	106	69	110	1.920	0.94	248	F8
240	4.188	-0.87	17	11	360	6.282	0.00	128	7F	120	2.094	0.87	239	EE
250	4.363	-0.94	8	7	10	0.175	0.17	150	96	130	2.269	0.77	226	E2
260	4.537	-0.98	2	1	20	0.349	0.34	172	AB	140	2.443	0.64	210	D2
270	4.712	-1.00	0	0	30	0.524	0.50	192	BF	150	2.618	0.50	192	C0
280	4.886	-0.98	2	1	40	0.698	0.64	210	D2	160	2.792	0.34	172	AB
290	5.061	-0.94	8	7	50	0.873	0.77	226	E2	170	2.967	0.17	150	96
300	5.235	-0.87	17	11	60	1.047	0.87	239	EE	180	3.141	0.00	128	80
310	5.410	-0.77	30	1D	70	1.222	0.94	248	F8	190	3.316	-0.17	106	69
320	5.584	-0.64	46	2D	80	1.396	0.98	254	FE	200	3.490	-0.34	84	54
330	5.759	-0.50	64	3F	90	1.571	1.00	256	FF	210	3.665	-0.50	64	40
340	5.933	-0.34	84	54	100	1.745	0.98	254	FE	220	3.839	-0.64	46	2D
350	6.108	-0.17	106	69	110	1.920	0.94	248	F8	230	4.014	-0.77	30	1E
360	6.282	0.00	128	7F	120	2.094	0.87	239	EE	240	4.188	-0.87	17	11

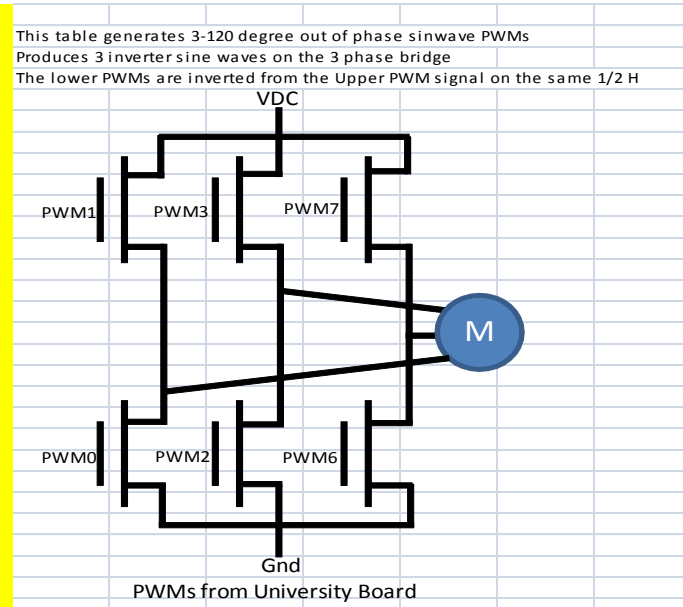

Phase Voltage and Current



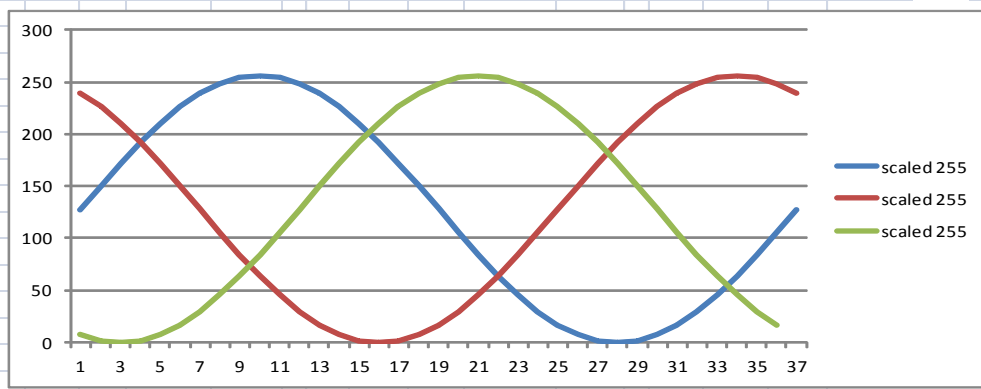Phase Voltage Phase Current Zero Crossing




Voltage Modulation

C D

deg	rad	Sin	100% Voltage	hex	C array	75% Voltage	50% Voltage	25% Voltage	hex	C array
0	0	0	128	80	0x8080,	128	128	128	80	0x8080,
5	0.087265	0.087154	139	8B	0x8B8B,	136	134	131	82	0x8282,
10	0.17453	0.173645	150	96	0x9696,	145	139	134	85	0x8585,
15	0.261795	0.258815	161	A1	0xA1A1,	153	145	136	88	0x8888,
20	0.34906	0.342015	172	AB	0xABAB,	161	150	139	8A	0x8A8A,
25	0.436325	0.422612	182	B6	0xB6B6,	169	155	142	8D	0x8D8D,
30	0.52359	0.499992	192	BF	0xBFBF,	176	160	144	8F	0x8F8F,
35	0.610855	0.573568	201	C9	0xC9C9,	183	165	146	92	0x9292,
40	0.69812	0.642779	210	D2	0xD2D2,	190	169	149	94	0x9494,
45	0.785385	0.707097	219	DA	0xDADA,	196	173	151	96	0x9696,
50	0.87265	0.766035	226	E2	0xE2E2,	202	177	153	98	0x9898,
55	0.959915	0.819143	233	E8	0xE8E8,	207	180	154	9A	0x9A9A,
60	1.04718	0.866017	239	EE	0xEEEE,	211	183	156	9B	0x9B9B,
65	1.134445	0.9063	244	F4	0xF4F4,	215	186	157	9D	0x9D9D,
70	1.22171	0.939686	248	F8	0xF8F8,	218	188	158	9E	0x9E9E,
75	1.308975	0.96592	252	FB	0xFBFB,	221	190	159	9E	0x9E9E,
80	1.39624	0.984804	254	FE	0xFEFE,	223	191	160	9F	0x9F9F,
85	1.483505	0.996193	256	FF	0xFFFF,	224	192	160	9F	0x9F9F,
90	1.57077	1	256	FF	0xFFFF,	224	192	160	9F	0x9F9F,

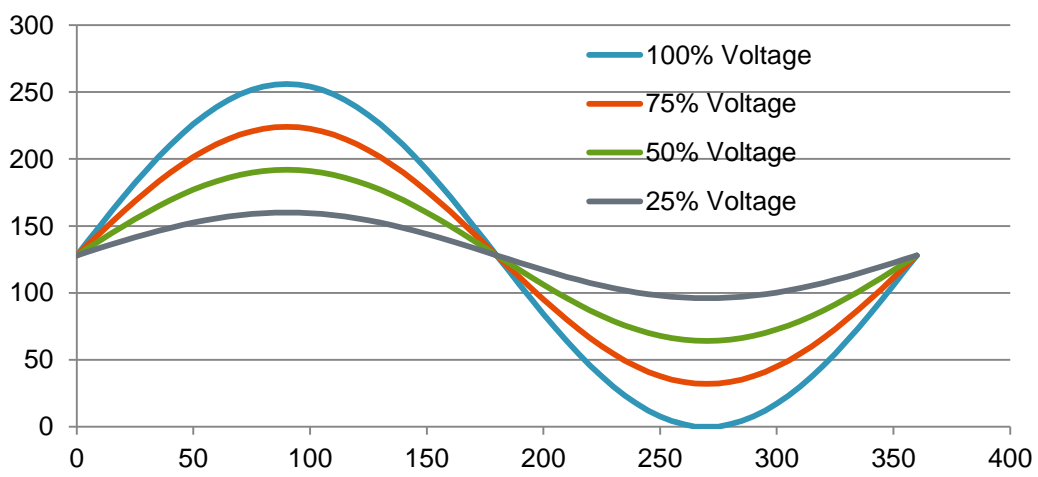← = "0x"&M2&M2&","
 Very useful for generating C arrays



=BIN2HEX(DEC2BIN(L2))

PWM = sin(i) * (0-1)*50%+50% *General Form*
 PWM = ((Cx * 0.75) * 128)+128 *Excel Form*
 PWM = ((Dx - 0x80)/voltlv)+0x80; *C Form*


50% is 1/2 of the PWM duty cycle. An 8bit duty cycle register is 256 (0xff). 50% is 128 (0x80)



3rd Harmonic For Greater Voltage


Fund	0	3rd	0	0	Sum of Fund & 3rd
0	0	0	0	0	0
5	0.087156	15	0.077646	0.164801	
10	0.173648	30	0.15	0.323648	
15	0.258819	45	0.212132	0.470951	
20	0.34202	60	0.259808	0.601828	
25	0.422618	75	0.289778	0.712396	
30	0.5	90	0.3	0.8	
35	0.573576	105	0.289778	0.863354	
40	0.642788	120	0.259808	0.902595	
45	0.707107	135	0.212132	0.919239	
50	0.766044	150	0.15	0.916044	
55	0.819152	165	0.077646	0.896798	
60	0.866025	180	3.68E-17	0.866025	
65	0.906308	195	-0.07765	0.828662	
70	0.939693	210	-0.15	0.789693	
75	0.965926	225	-0.21213	0.753794	
80	0.984808	240	-0.25981	0.725	
85	0.996195	255	-0.28978	0.706417	
90	1	270	-0.3	0.7	
95	0.996195	285	-0.28978	0.706417	
100	0.984808	300	-0.25981	0.725	
105	0.965926	315	-0.21213	0.753794	
110	0.939693	330	-0.15	0.789693	
115	0.906308	345	-0.07765	0.828662	
120	0.866025	360	-7.4E-17	0.866025	
125	0.819152	375	0.077646	0.896798	
130	0.766044	390	0.15	0.916044	
135	0.707107	405	0.212132	0.919239	
140	0.642788	420	0.259808	0.902595	
145	0.573576	435	0.289778	0.863354	
150	0.5	450	0.3	0.8	
155	0.422618	465	0.289778	0.712396	
160	0.34202	480	0.259808	0.601828	
165	0.258819	495	0.212132	0.470951	
170	0.173648	510	0.15	0.323648	
175	0.087156	525	0.077646	0.164801	
180	1.23E-16	540	1.1E-16	2.33E-16	

3rd Harmonic

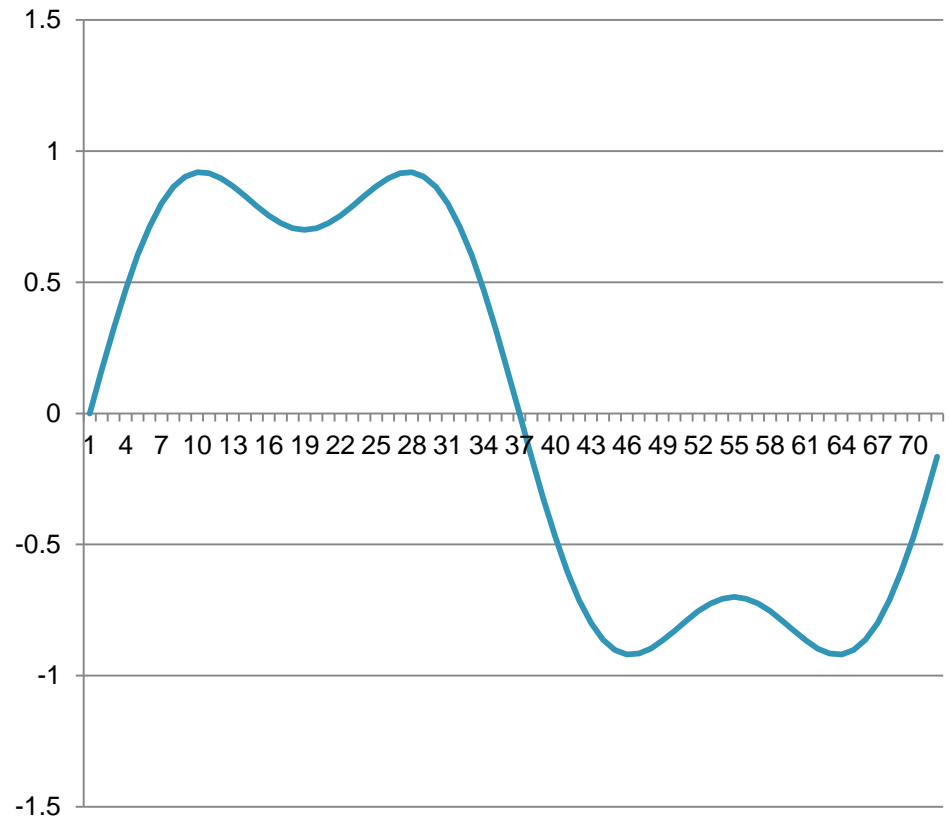

Sinusoidal Modulation - Limited in Amplitude

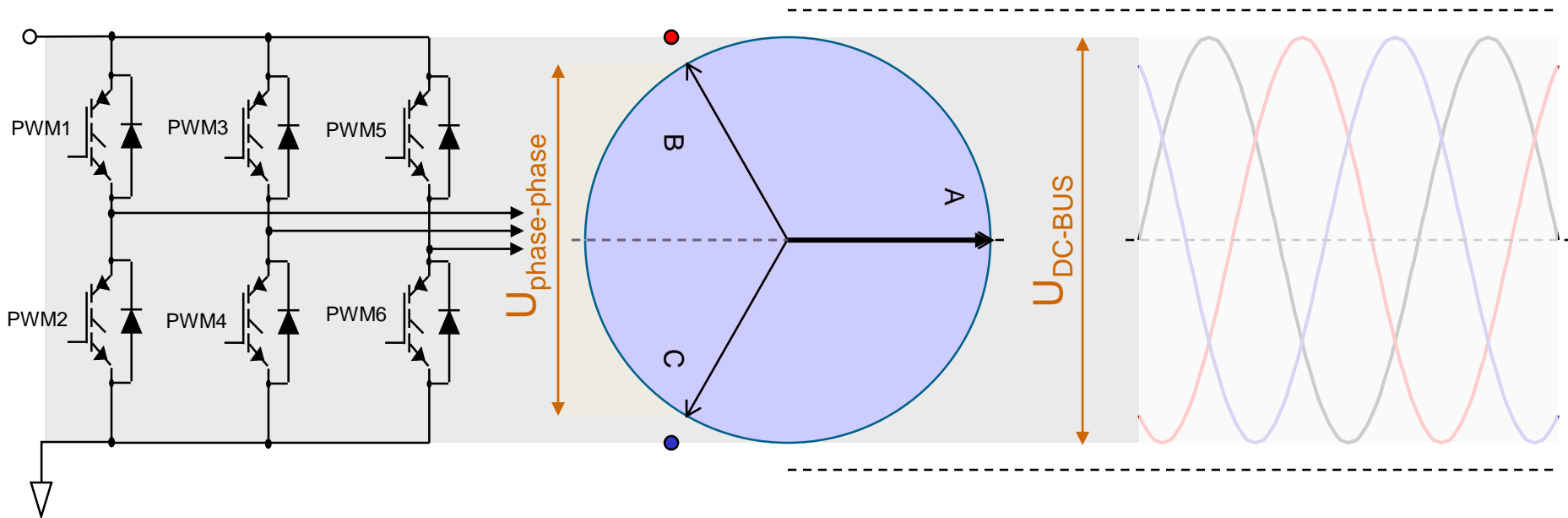
- In sinusoidal modulation the amplitude is limited to half of the DC-bus voltage.
- The phase to phase voltage is then lower than the DC-bus voltage (although such voltage can be generated between the terminals).



Can there be found such modulation technique that would generate full phase-to-phase voltage ?

Full Phase-to-Phase Voltage Generation

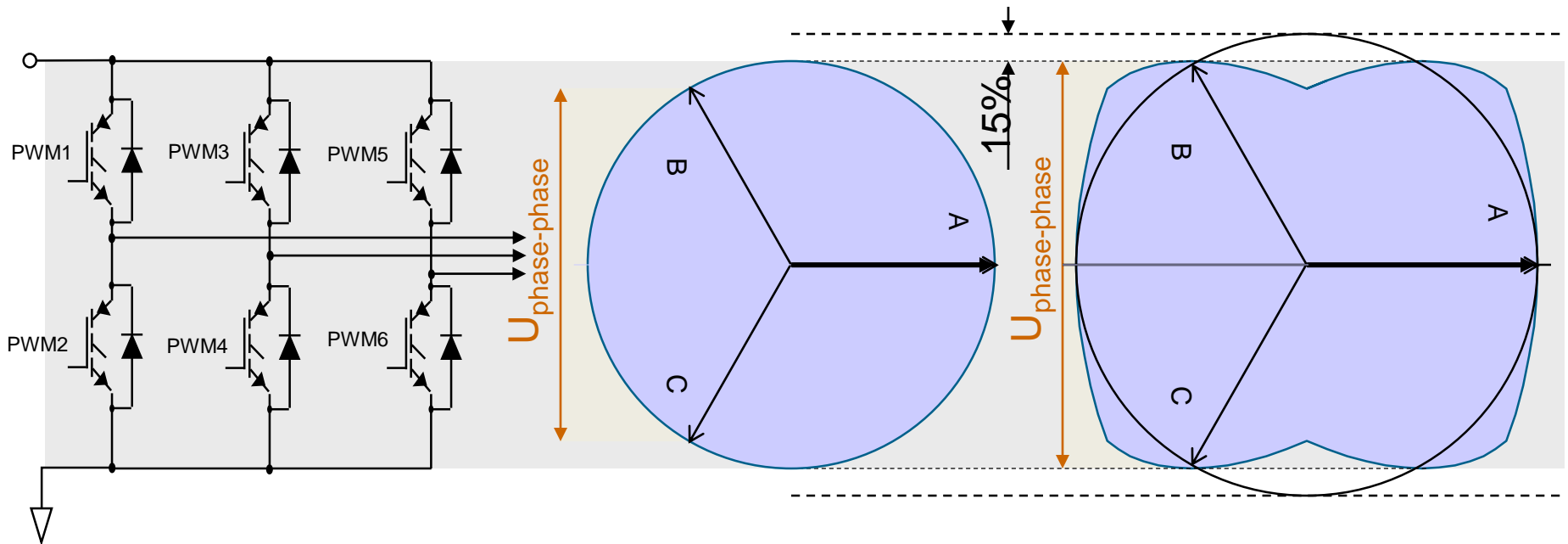- Full phase-to-phase voltage can be generated by continuously shifting the 3-phase voltage system.
- The amplitude of the first harmonic can be then increased by 15.5%.



Voltage to Frequency Table for a 230V 60Hz Induction Motor

- The V/F ratio must be maintained fairly closely
- A 230V 60Hz motor has a ratio of 3.83.

How Many Lines of C Code will it take to commutate the Induction Motor?

Volts	HZ	Period ms
230	60.00	16.67
220	57.39	17.42
210	54.78	18.25
200	52.17	19.17
190	49.57	20.18
180	46.96	21.30
170	44.35	22.55
160	41.74	23.96
150	39.13	25.56
140	36.52	27.38
130	33.91	29.49
120	31.58	31.67
110	28.95	34.55
100	26.32	38.00
90	23.68	42.22
80	21.05	47.50
70	18.42	54.29
60	15.79	63.33
50	13.16	76.00
40	10.53	95.00
30	7.89	126.67
20	5.26	190.00

Induction Freq. & Voltage Control

```
word sine[72]={0x8080, 0x8B8B ,0x9696 ,0xA1A1 ,0xABAB ,0xB6B6, 0xBFBF ... ,0xEEEE ,0xF4F4 ,0xF8F8 ,0xF9F9 ,0xF9F9 ,0xFaFa ,0xFFFF
for(i=0; i<=71; i++) /* walk through the array */

{
    j=(i+24)%72;      /* offsets j 120 degrees from i this is for the 5 degree table 72 elements */
    k=(i+48)%72;      /* offsets k 240 degrees from i this is for the 5 degree table 72 elements */

    vardly();          /* POT1 sets the fundamental frequency */

    /***** voltage control *****/
    tempi = sine[i];
    tempj = sine[j];
    tempk = sine[k];

    if (ATD1DR1H < 0x40) voltlv = 4; else if (ATD1DR1H < 0x80 ) voltlv = 2; else voltlv = 1; /* sets the voltage at 100% or 50% or 25% */

    tempi= (((tempi&0x00ff)-0x80)/voltlv)+0x80;      /* based on voltlv = 1 or 2 scale the pwm phase i */
    tempi = tempi & 0x00ff;
    tempi = tempi + (tempi << 8);

    tempj= (((tempj&0x00ff)-0x80)/voltlv)+0x80;      /* based on voltlv = 1 or 2 scale the pwm phase j */
    tempj = tempj & 0x00ff;
    tempj = tempj + (tempj << 8);


    tempk= (((tempk&0x00ff)-0x80)/voltlv)+0x80;      /* based on voltlv = 1 or 2 scale the pwm phase k */
    tempk = tempk & 0x00ff;
    tempk = tempk + (tempk << 8);

    PWMDTY01 = tempi;          /* write PWMs 0&1 */
    PWMDTY23 = tempj;        /* write PWMs 2&3 */
    PWMDTY67 = tempk;        /* write PWMs 3&4 */
}
}
```

Inverter Hardware






GDB Test Inverter GD3100 Block Interface

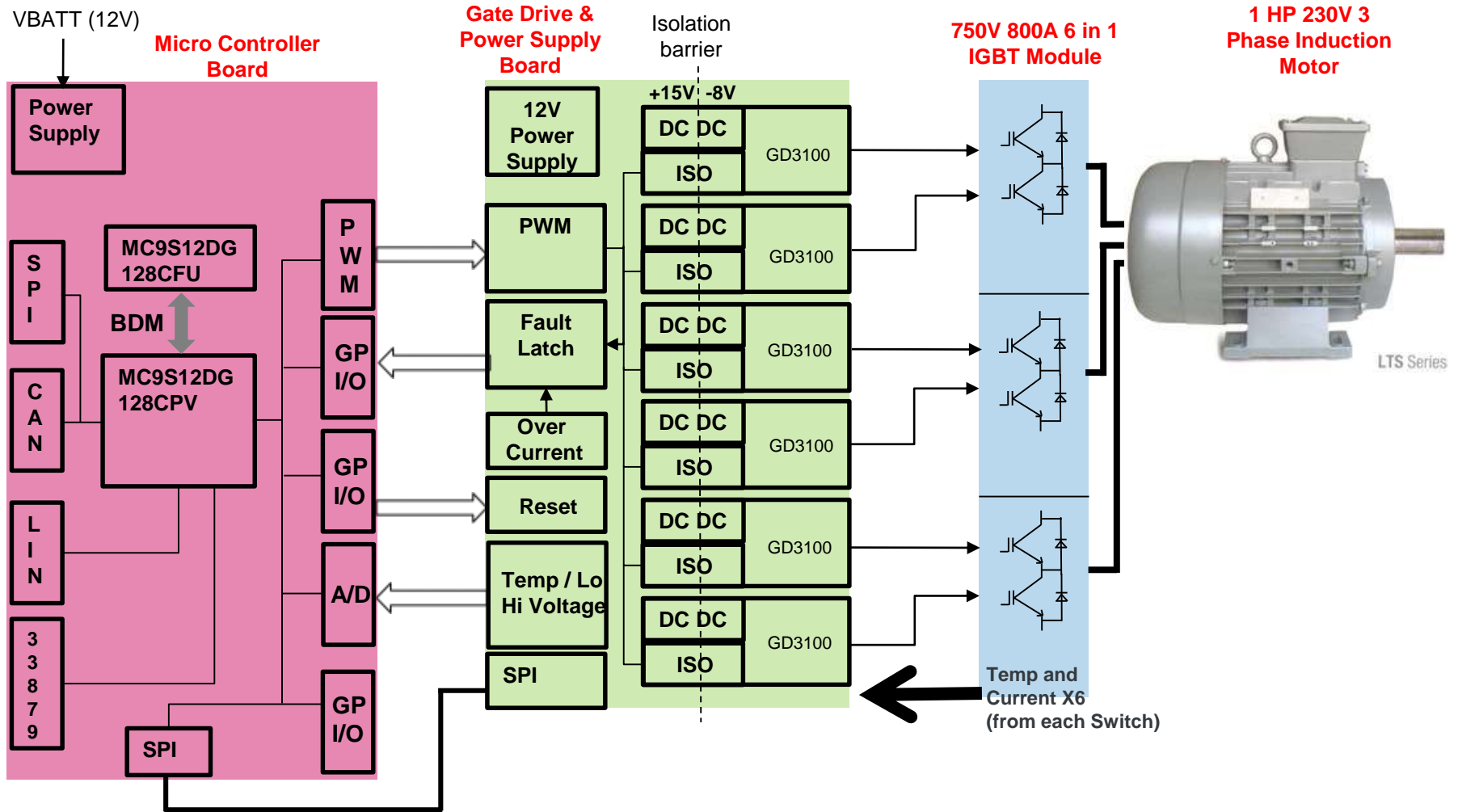


3ph AC voltage generation on a per phase basis

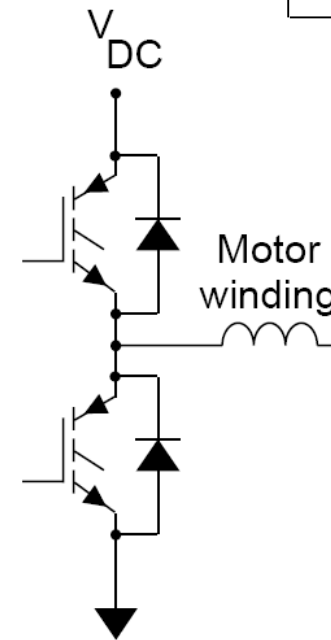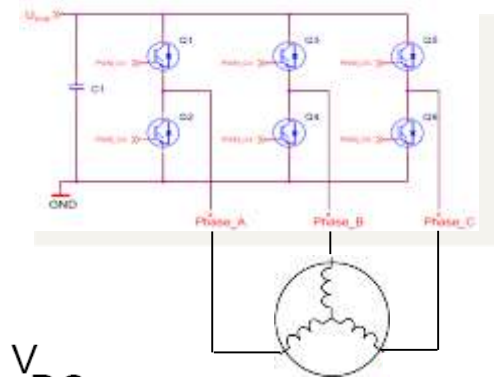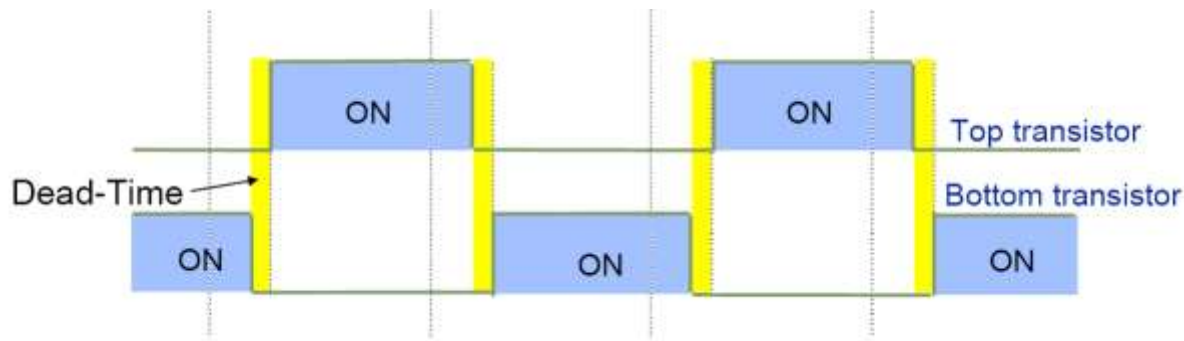
- Each phase is considered a “Half H-Bridge”
- Complementary PWMs are used
- Deadtime is needed to prevent shoot through.
- 50% duty cycle → Zero voltage on phase winding



Dead Time – A Necessary Evil But....

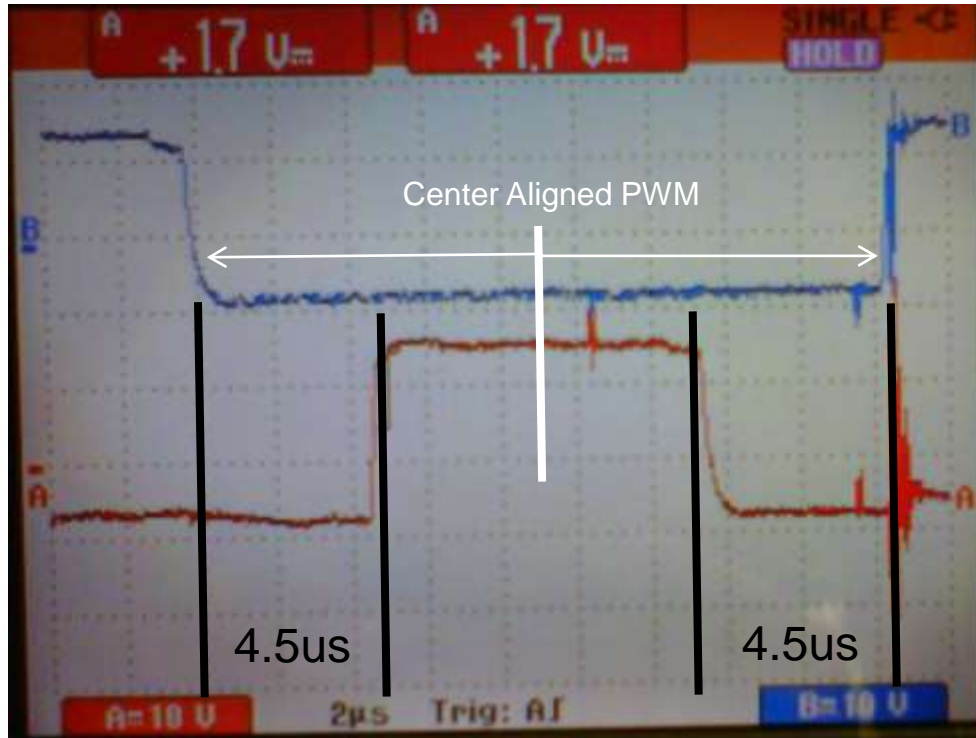

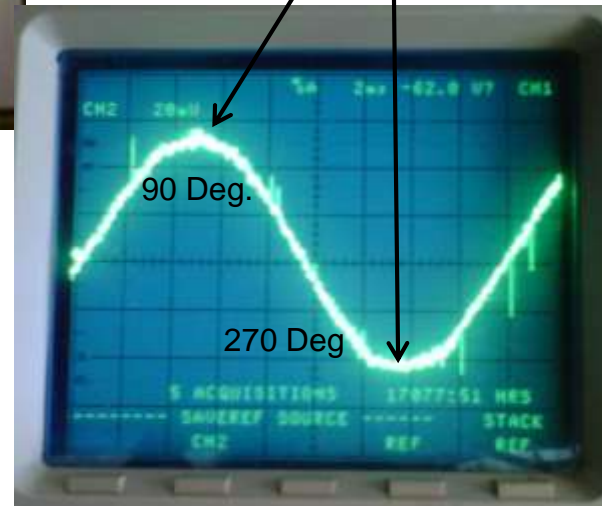- 10KHz PWM
- 100us Period
- 8-bit Duty Cycle PWM(255)
- 1-bit time = .39us
- @ 4.5us D.T. you lose 10 counts!




Dead time causes distortion in the current waveform but It can be corrected!

Deg.	C array
70	0xF8F8,
75	0xFBFB,
80	0xFEFE,
85	0xFFFF,
90	0xFFFF,
95	0xFFFF,
100	0xFEFE,
105	0xFBFB,
110	0xF8F8,



750V 800A IGBT and GDB

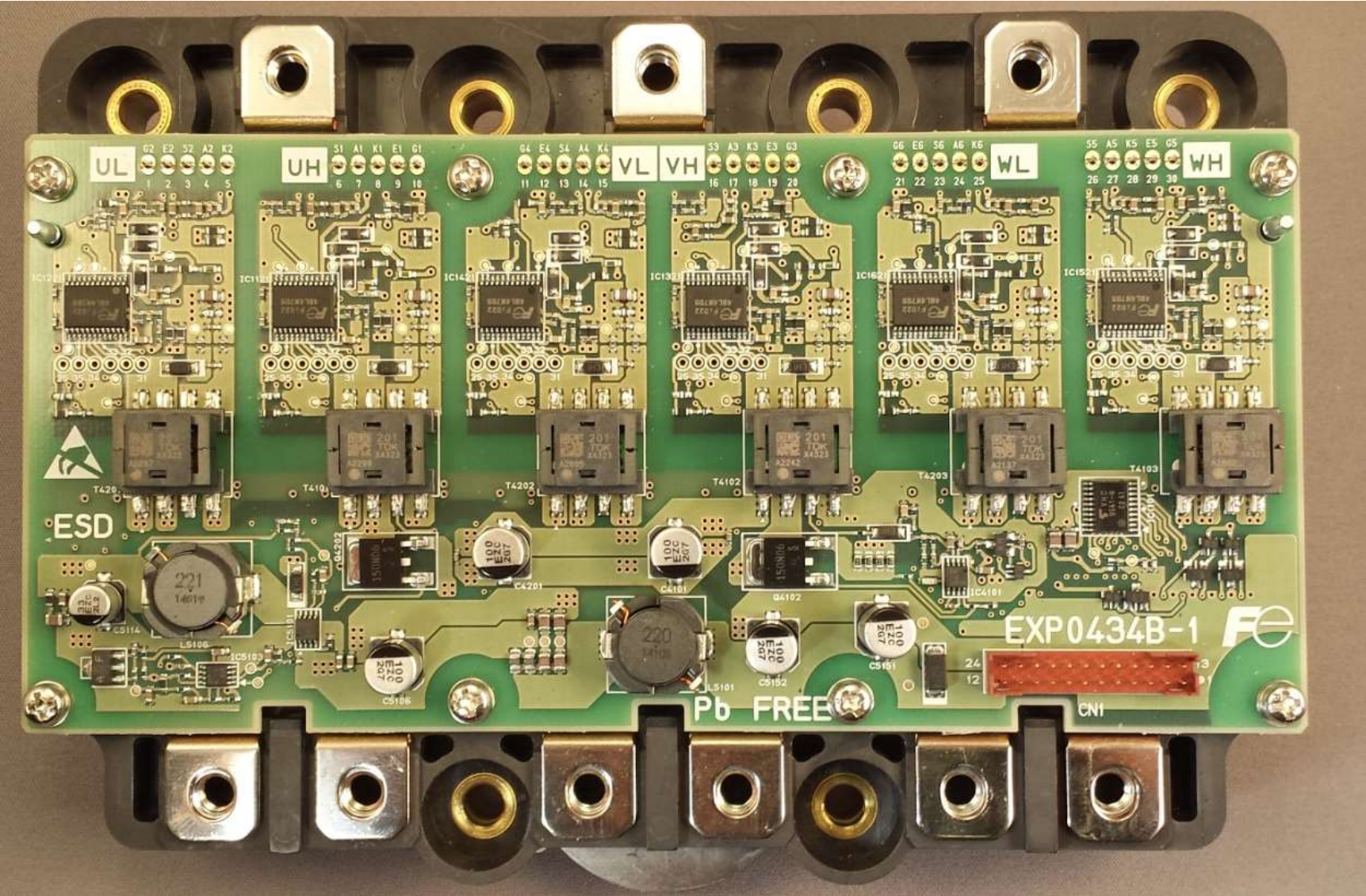


EXP0434 Gate Drive Board for Fuji M653 Power Module uses Fuji's Fi022 gate drive IC

- Size: 161mm long, 76 mm wide
- Status: Demonstration board only, not intended for mass production
- EEPROM: Pins for trimming. Required to attain +/- 3 °C accuracy at high temperature.
- GICL: Not implemented on Fi022 GDIC but provided with 3 optocouplers for each IGBT switch (18 total)
- Gate Supplies: Positive gate supply only. No provision for negative gate supply.
- Significant VBATT filtering
- Two flyback switchers servicing 3 transformers each. Voltage feedback provided by auxiliary winding.
- Low powered buck converter to power logic on the non-isolated side
- External transistors for each gate drive
- Short circuit faults are detected only by monitoring current sense features. No provision for Vce desaturation detection.
- No emergency supply, no monitoring of DC_Link voltage, specific fault information not available, no BIST, etc.




EXP0434 Gate Drive Board for Fuji M653 Power Module

uses Fuji's Fi022 gate drive IC

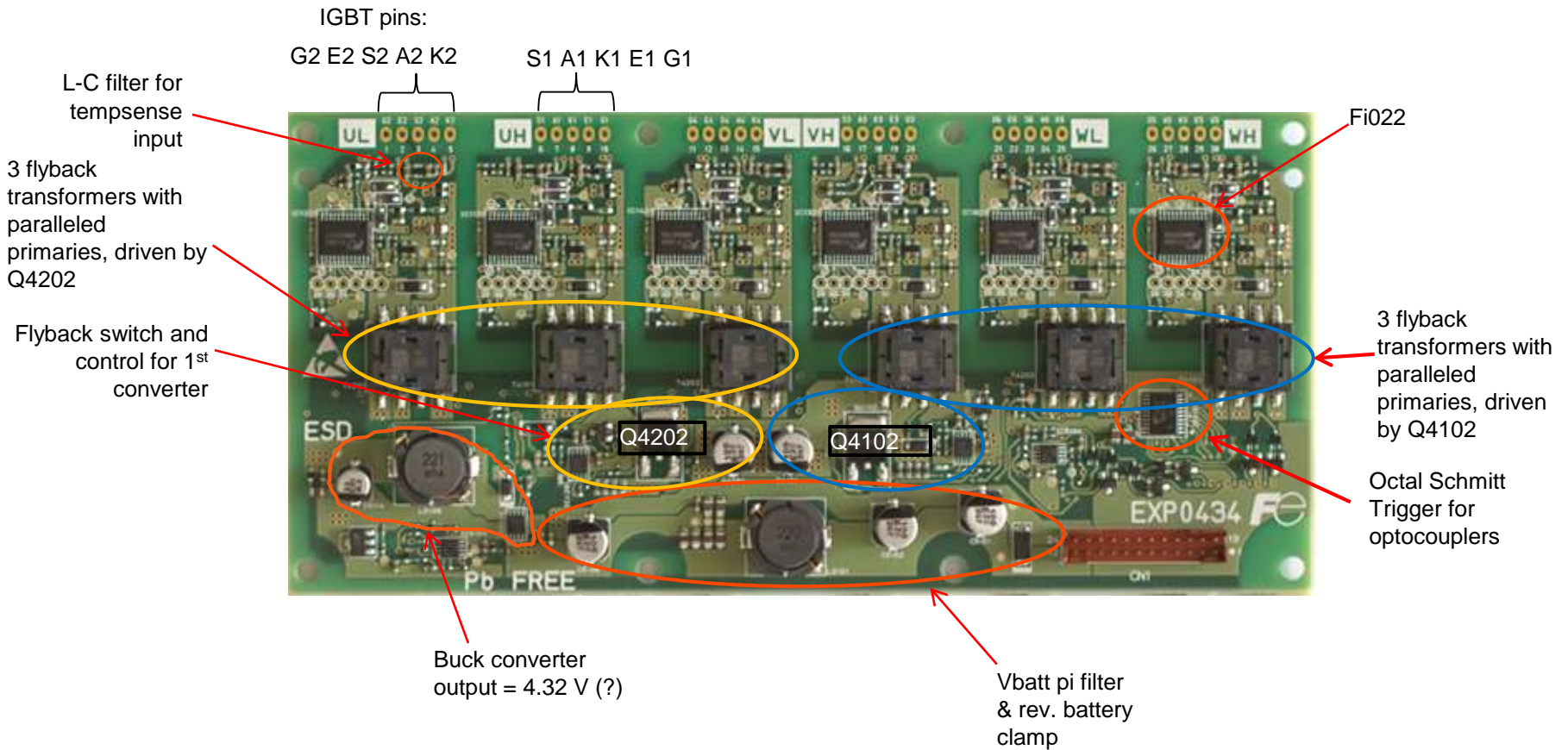


EXP0434 Gate Drive Board for Fuji M653 Power Module

uses Fuji's Fi022 gate drive IC

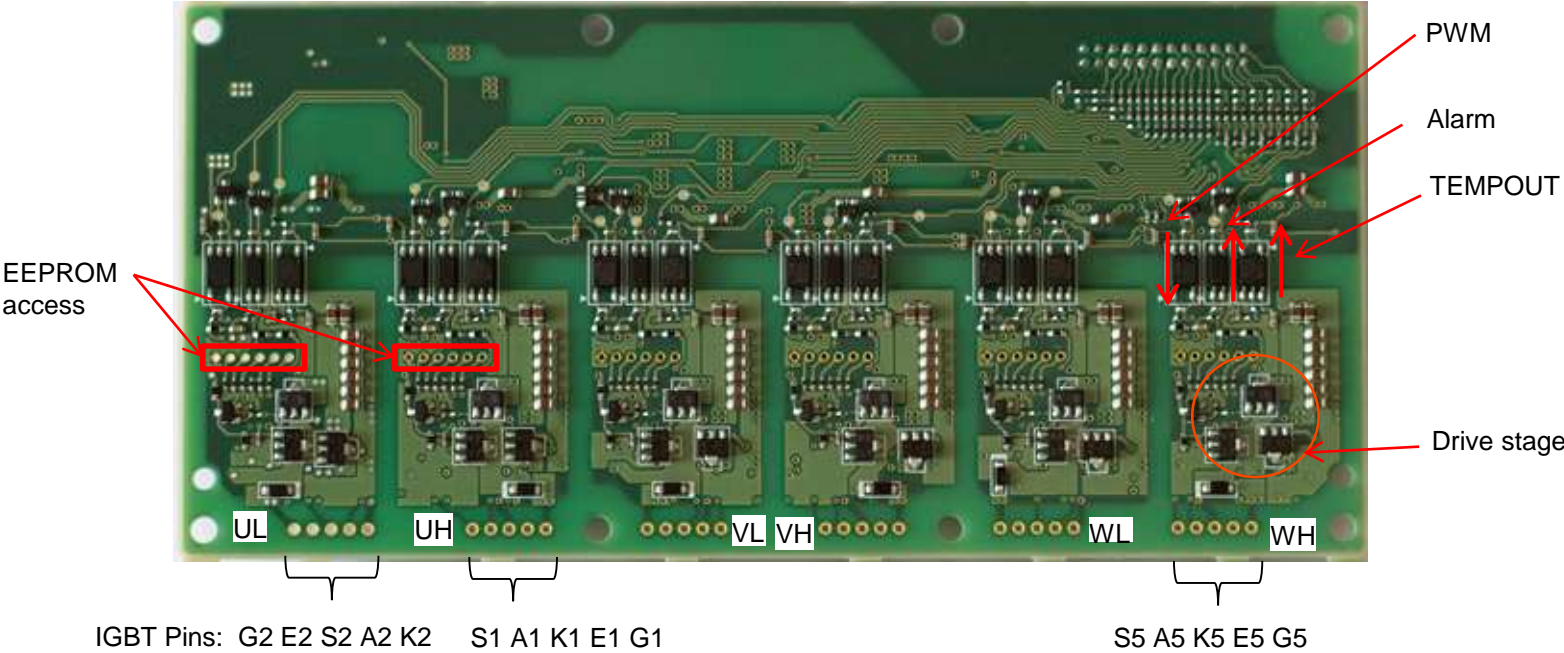


Challenges of Inverter Design

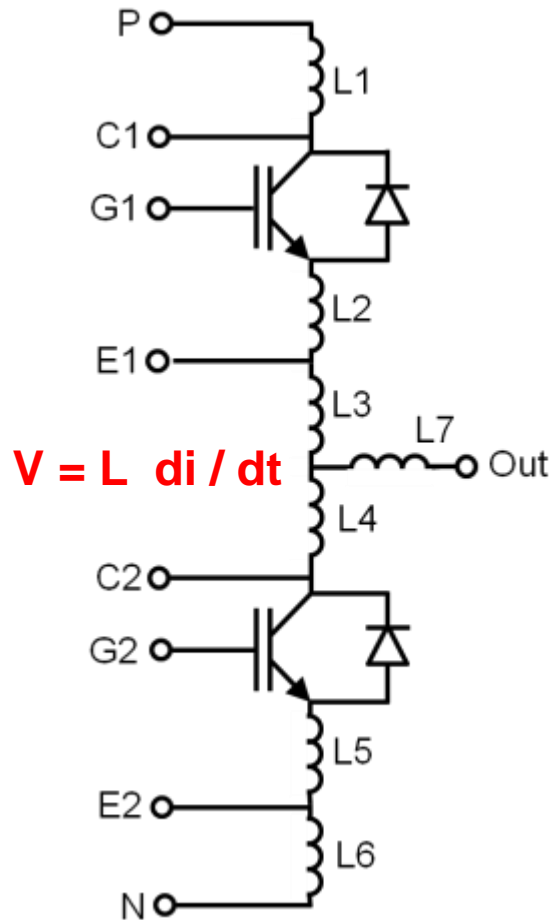

- L2 and L5 are small inductances (~1nH, typical) that are common to the gate drive as well as the emitter. These inductances slow turn on and turn off because their induced voltages negatively affect the desired voltage appearing at the gate-emitter terminals of the die.
- The 6MBI400VN-065V has a total phase inductance (sum of L1 through L6) of about 28nH.
- IGBTs require breakdown voltages much higher than the bus supply voltage because high di/dt during switching is creating additional voltage at the IGBT die. The higher breakdown voltage requirements are increasing die cost.
- Externally, you could see at least an additional 20nH for the bus bars and 15nH for the input capacitor.
- **At 5A / ns and 63nH you could see a 315V overshoot. With a 400V battery bus you would need a 750V device, and it gets worse at cold!**

6MBI400VN-065V Turn-off Characteristics

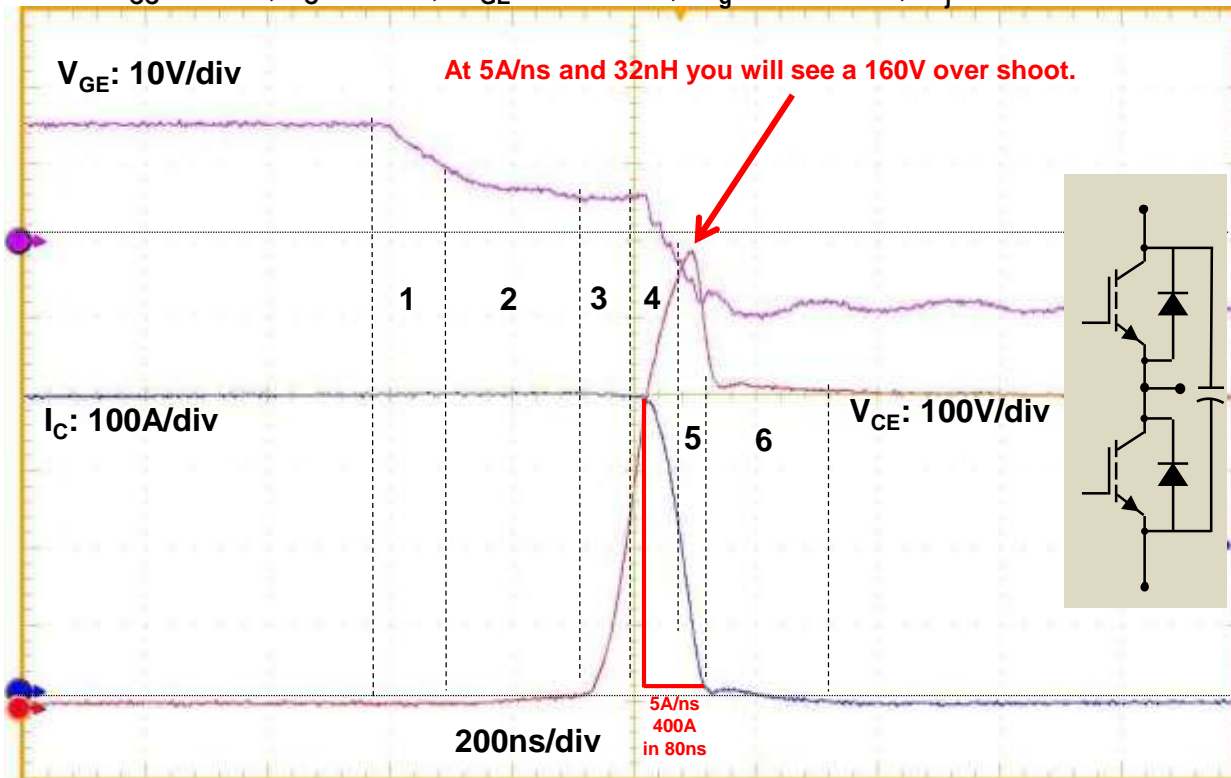
$V_{CC} = 400V$, $I_C = 400A$, $V_{GE} = +15V/8V$, $R_g = +3.9/12\Omega$, $T_j = 25^\circ C$



- 1 - V_{GE} begins to discharge
- 2 - V_{CE} begins to change. It rises very slowly since the gate drive is charging C_{CG} , which is very large at this time.
- 3 - V_{CE} rises much more rapidly since C_{CG} is much smaller at this time. I_C does not yet change since the opposing diode is not forward biased.
- 4 - Output current is commutated to the opposing diode as the IGBT turns off.
- 5 - Peak V_{CE} voltage falls as di/dt decreases. Diode is now conducting all the output current.
- 6 - IGBT current decays as carriers within the IGBT recombine.

From: Fuji's "Device features of the 6MBI400VN-065V_03-June-2011.pdf"

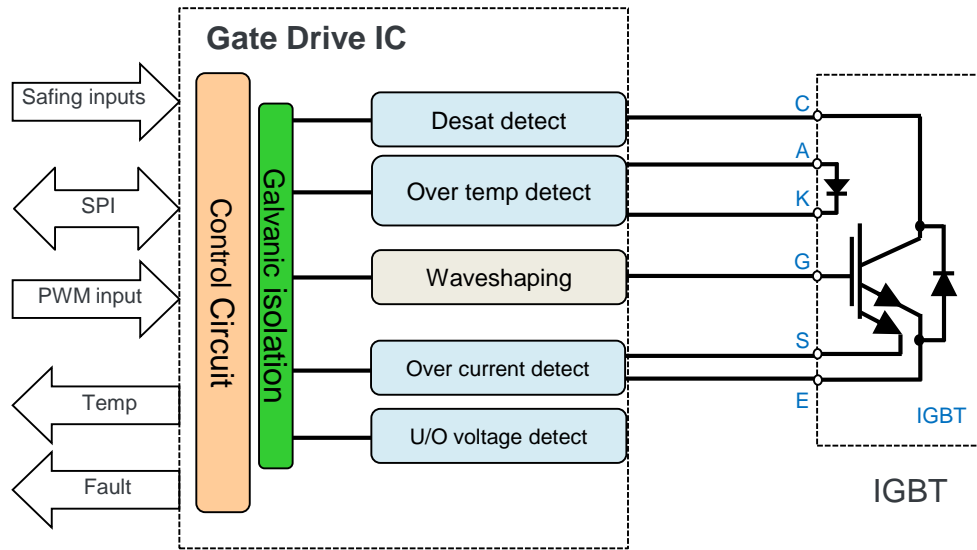Freescale Driver ↔ Fuji GEN7 IGBT System Integration



Benefits of GD3100 optimized for Fuji's IGBTs:

Desat, temperature and over current direct feedback:

- Enables high speed over current protection minimizing IGBT stress
- Increases system reliability and protection against catastrophic failure
- Allows monitoring IGBT degradation in real time
- Eliminates need for complex external protection circuitry

Waveshaping:

- Active Miller clamp eliminates need for negative gate supply voltage
- Integration of high power (10A) stage for increased system efficiency

Integrated Galvanic Isolation:


- Protection from high voltage
- Allows for compact modules

SPI interface:

- For safety monitoring, programmability and flexibility

Fuji M653 750V 800A Gen. 7 6in1

Fuji Gen. 7

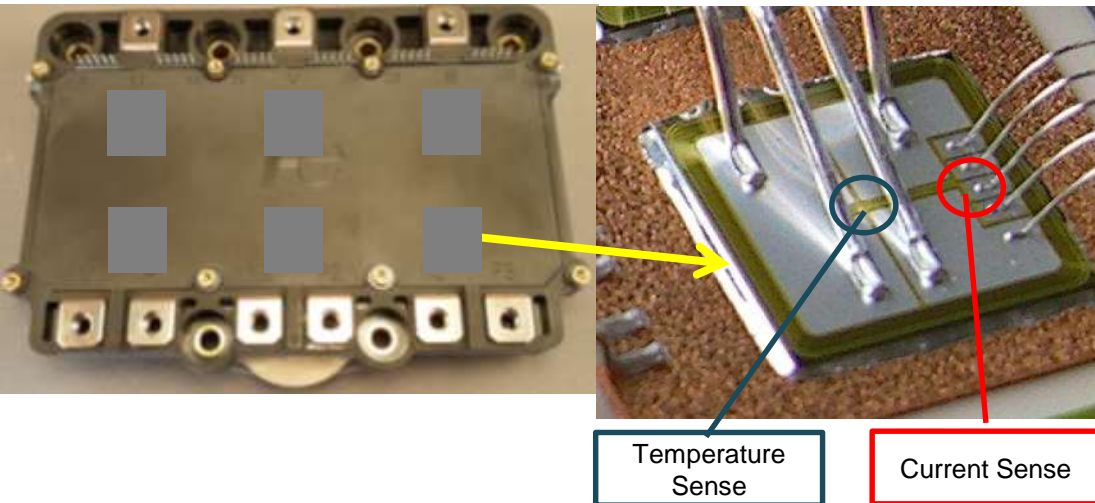


Temperature Sense


Current Sense

■ High reliability : On-chip current sensor

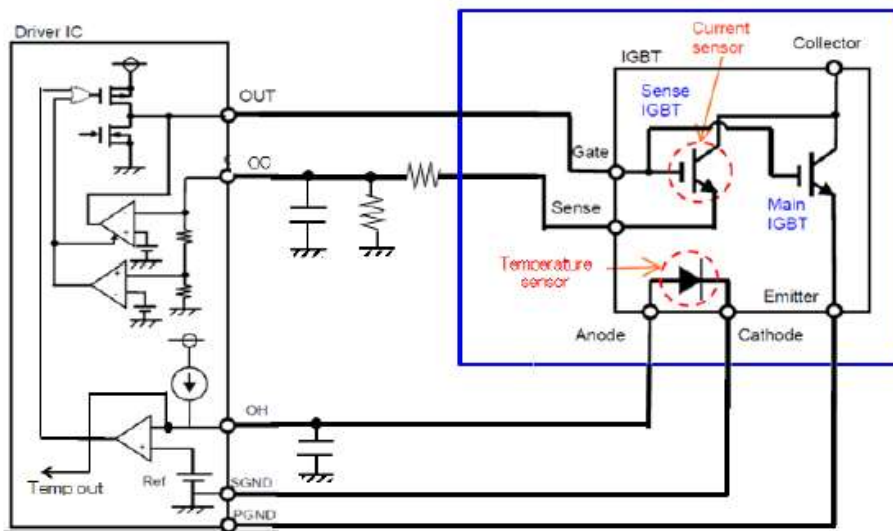
- ◆ By using on-chip current sensing IGBT, over current can be suppressed in a short time.
- ◆ In the short circuit situation, over current is controlled accurately.
- ◆ Reduced stress on the IGBT minimizes the risk of failure.
- ◆ Reduced Market failure rate.



Short circuit operation

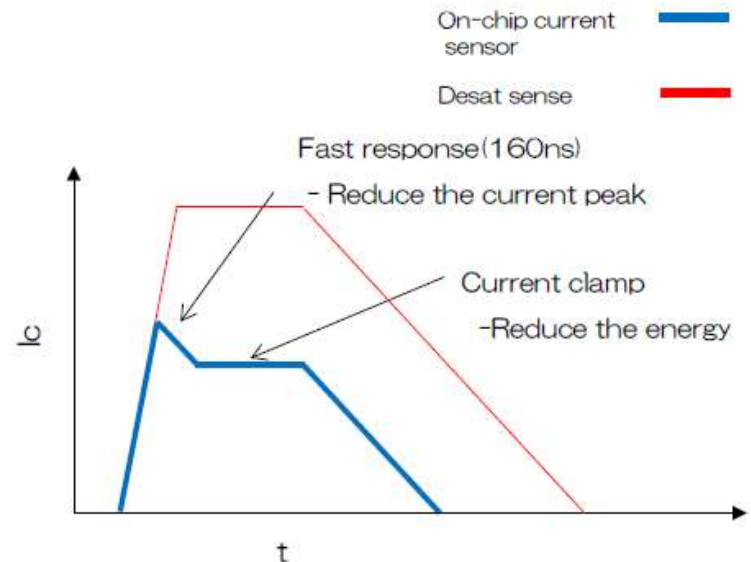


Simplified Application Schematic

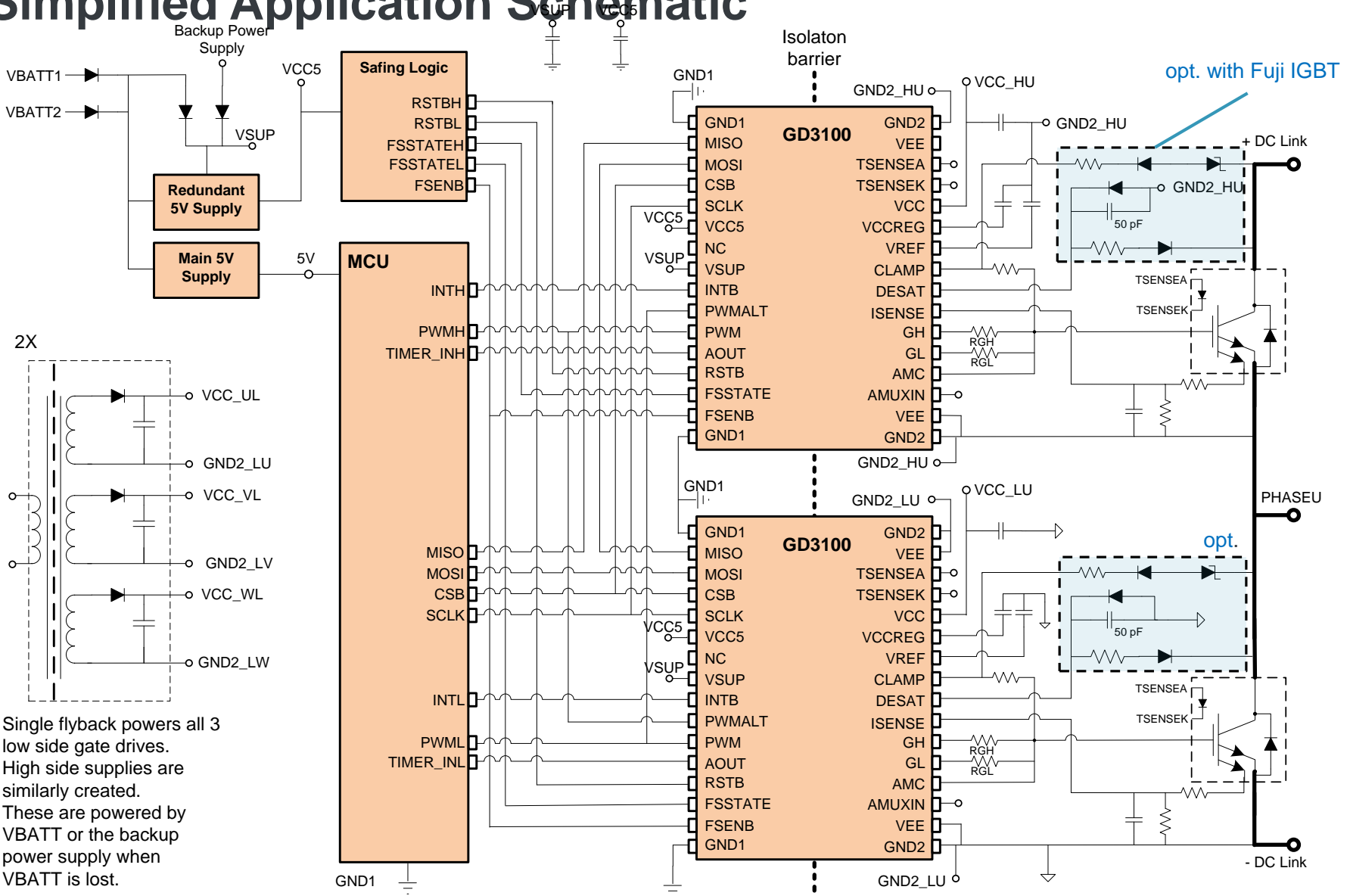


Single flyback powers all 3 low side gate drives. High side supplies are similarly created. These are powered by VBATT or the backup power supply when VBATT is lost.




System Simplification & Savings

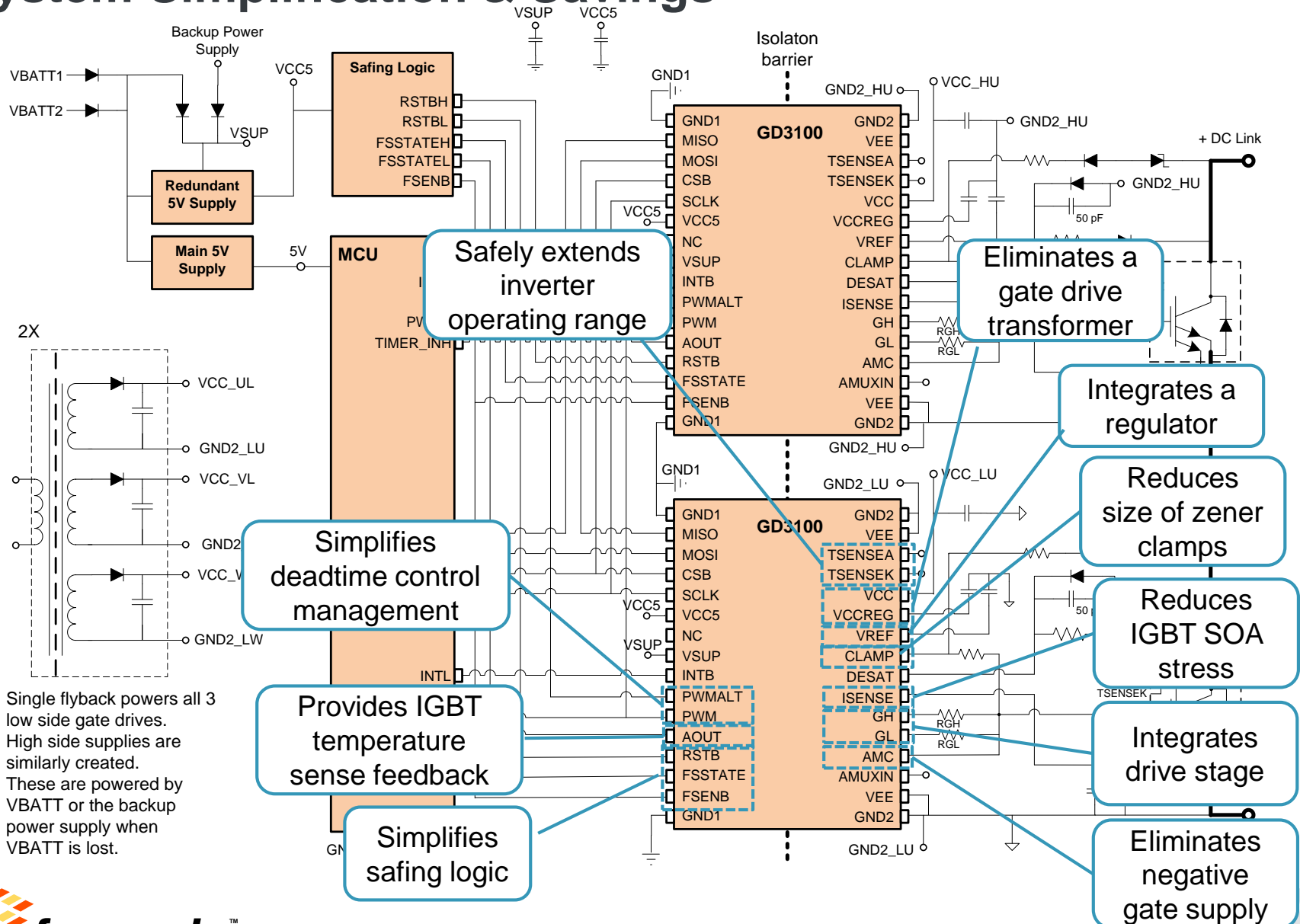


FreeMASTER controlling the inverter

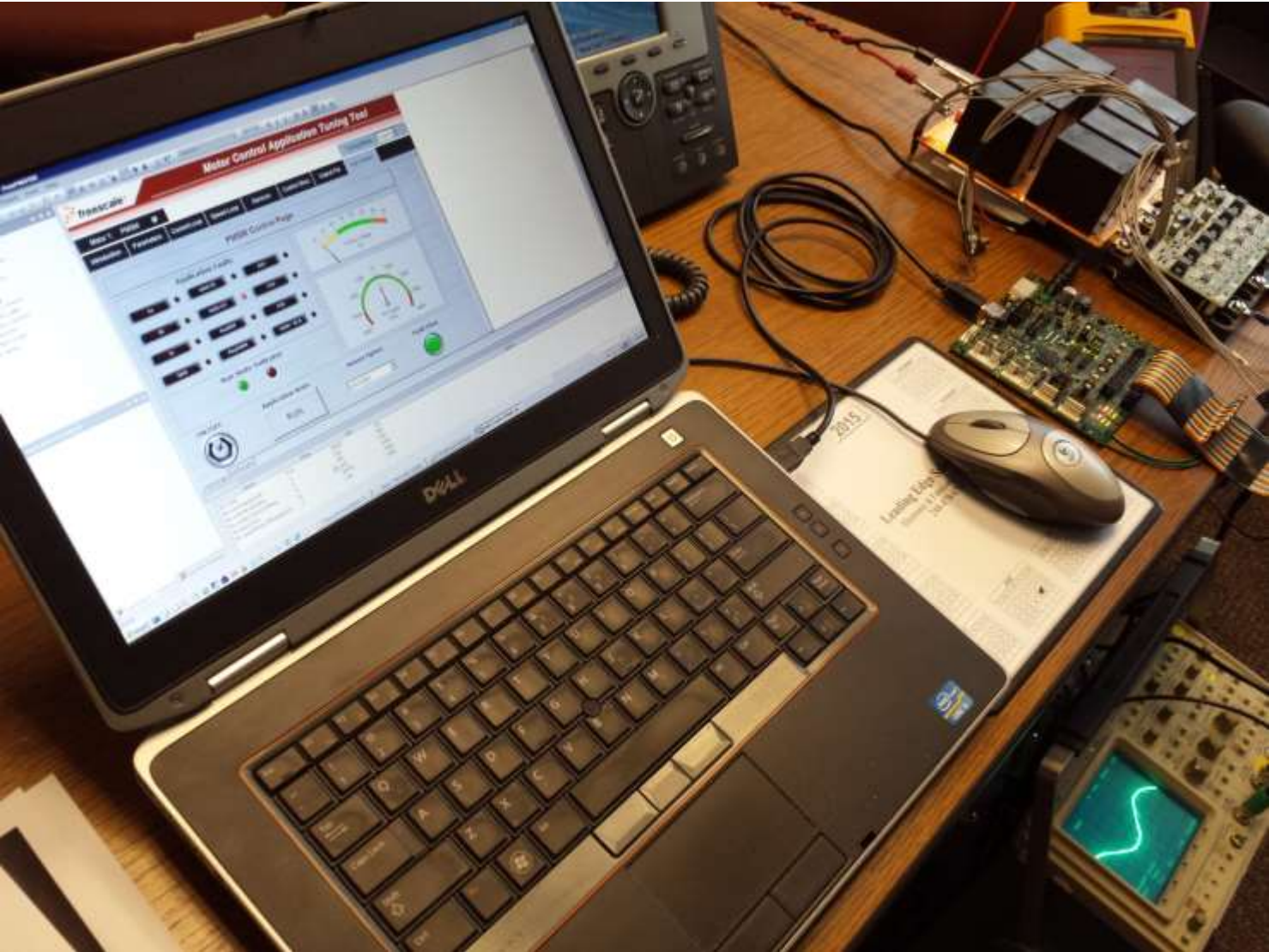

125kW Inverter with Fuji Gen. 7 Silicon

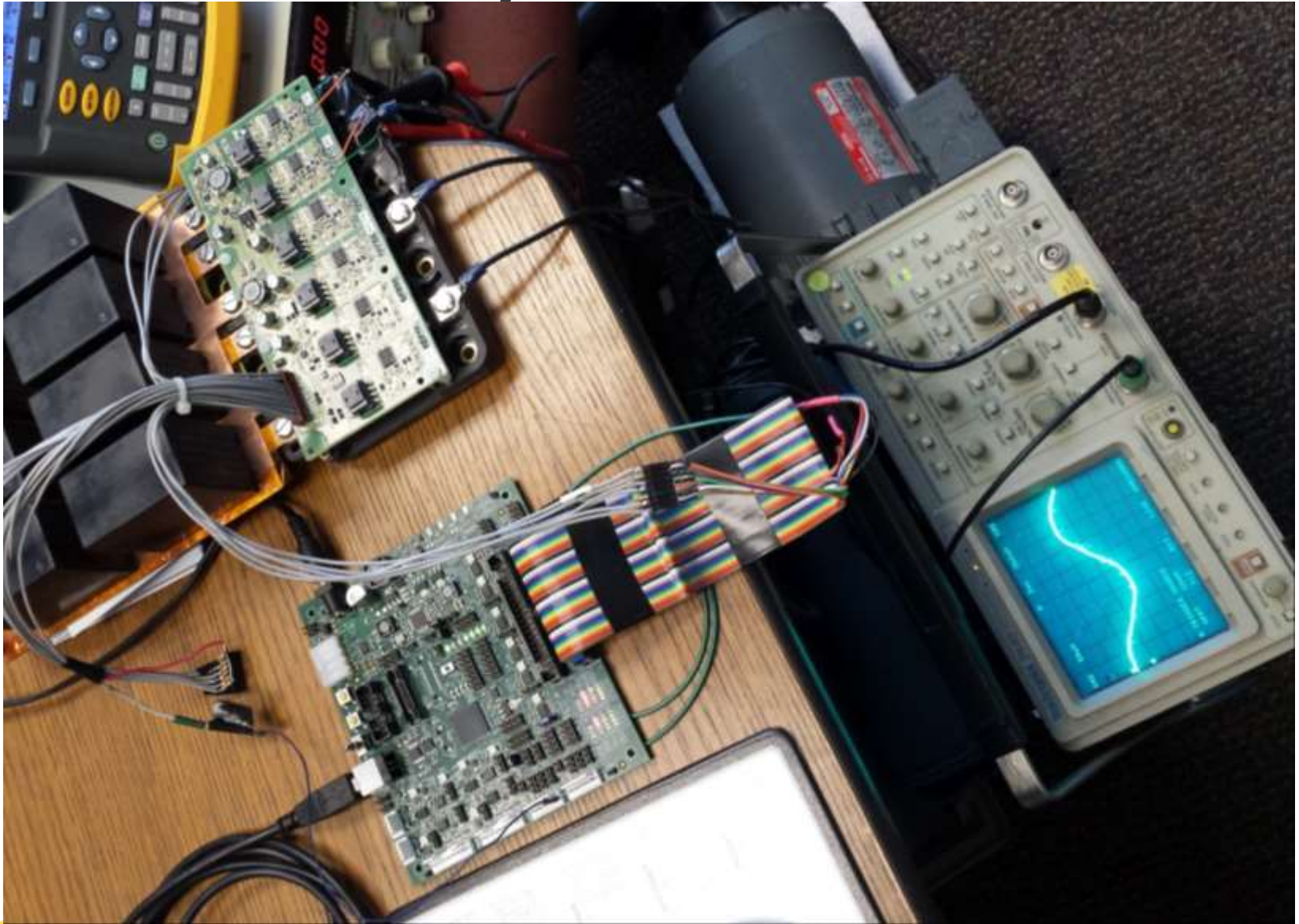

40KW Modular Inverter Reference Design

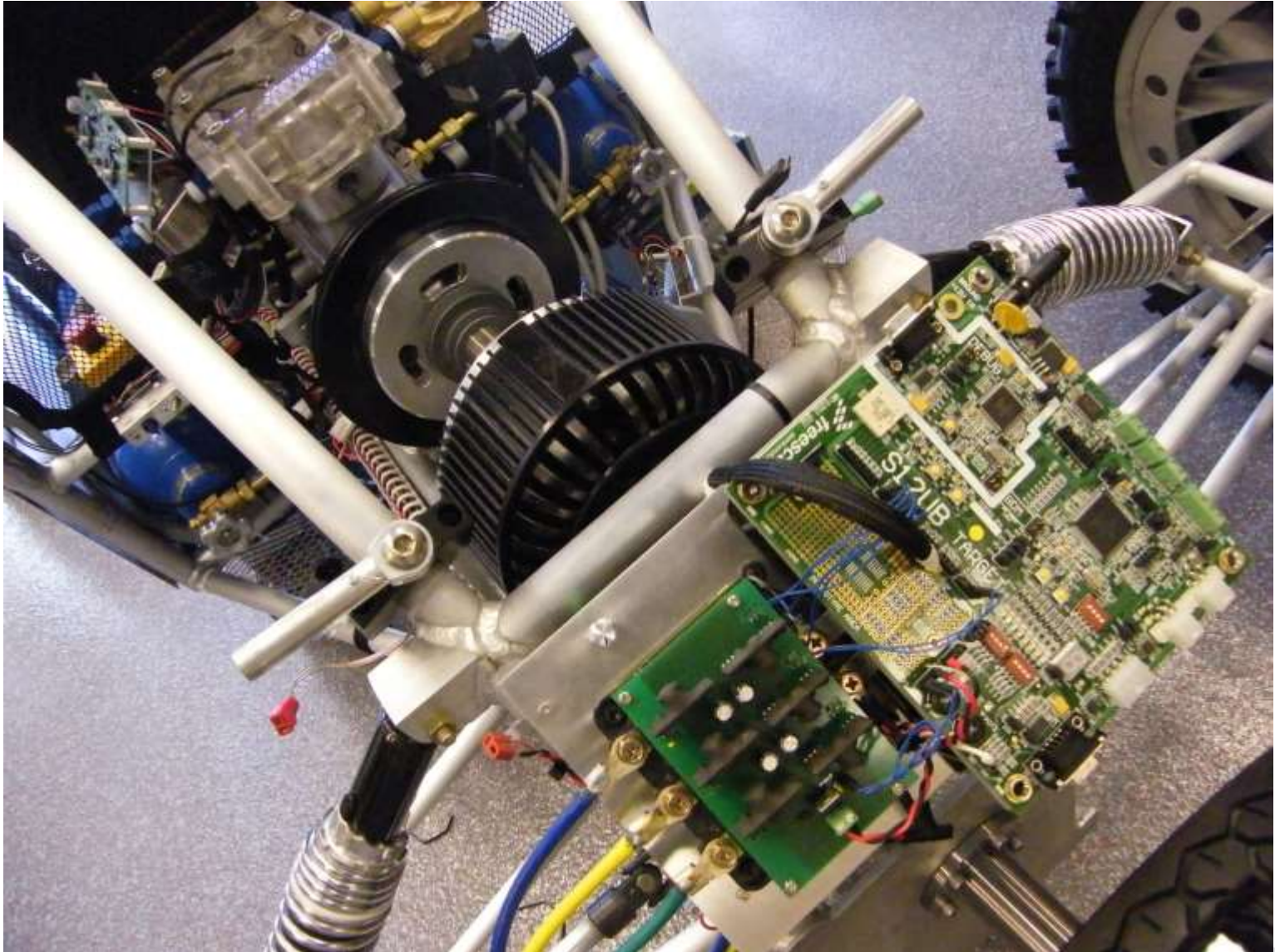

Stop by the Concept Vehicle in the Tech Lab





www.Freescale.com